
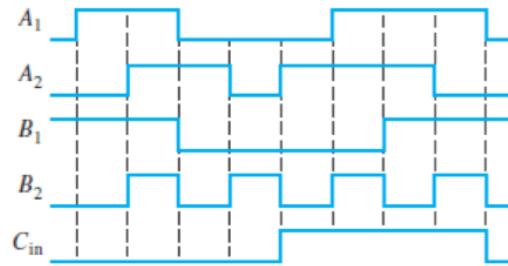



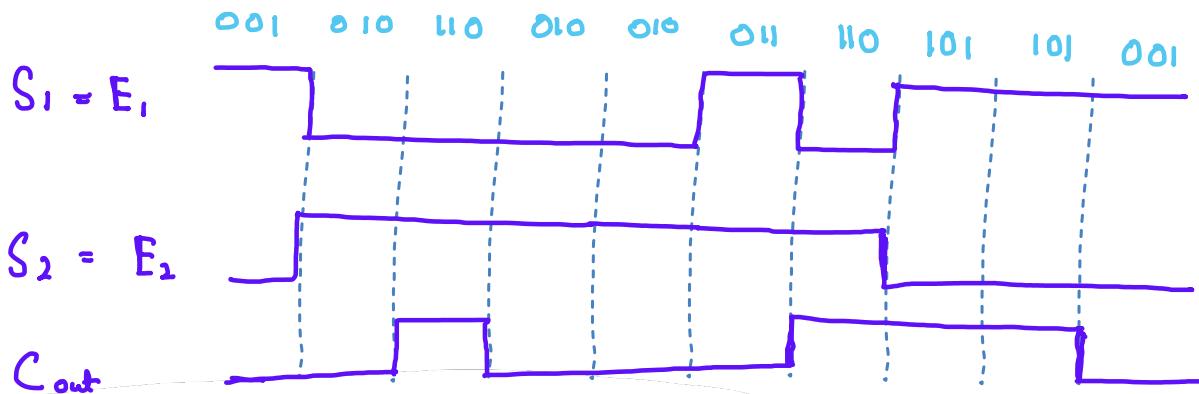
1. The input waveforms in Figure are applied to a 2-bit adder. Determine the waveforms for the sum and the output carry in relation to the inputs by constructing a timing diagram.



Sol:



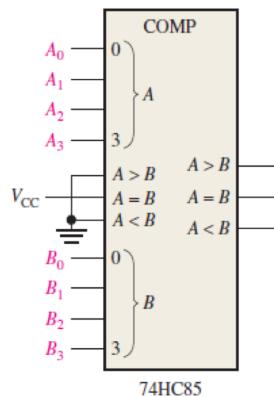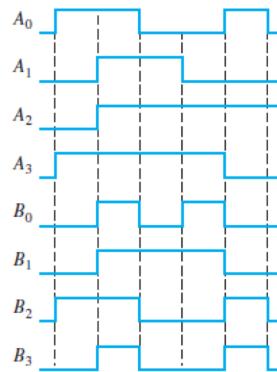2. For the 4-bit comparator in Figure, plot each output waveform for the inputs shown. The outputs are active-HIGH.




Sol:



$A < B$

$A = B$

$A > B$

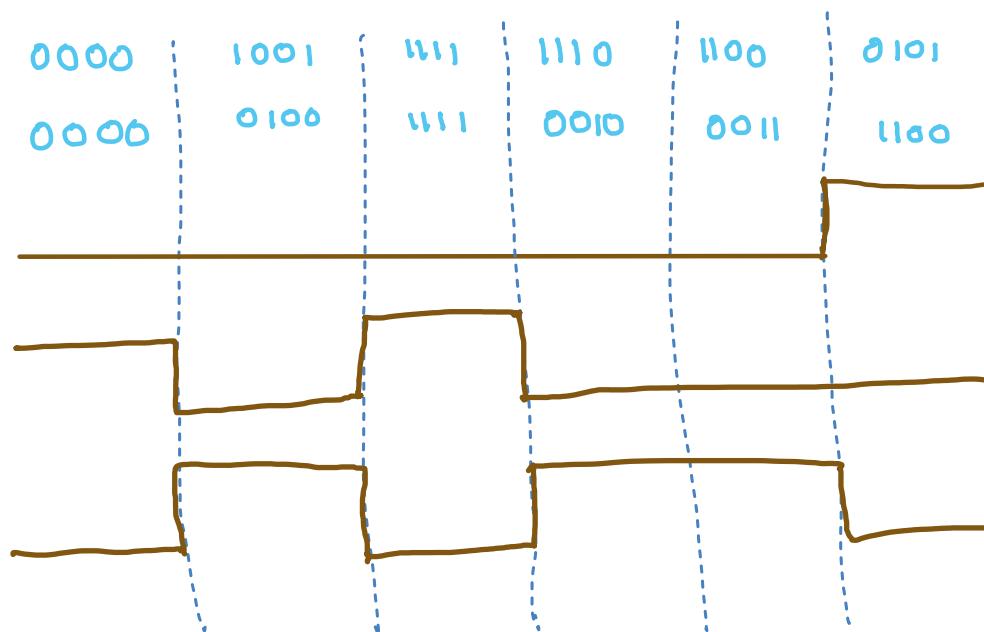


3. Show the decoding logic for each of the following codes if an active-HIGH (1) output is required: (a) 1101 (b) 1000 (c) 11011 (d) 11100

Sol:


(i) 1101

$A B \bar{C} D$

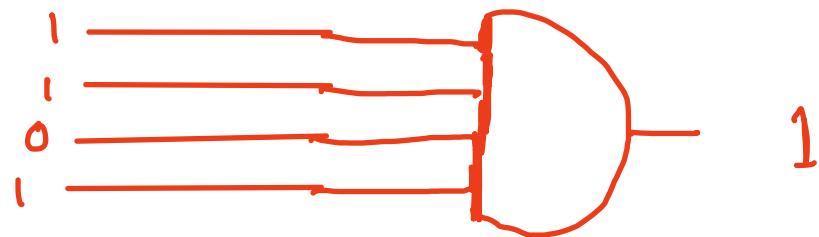


(iii) 11011

$A B \bar{C} \Delta F$

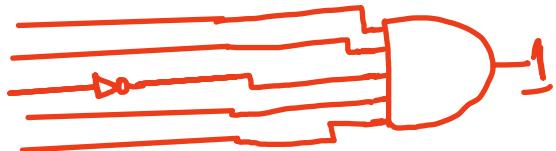


(ii) 1000

$A \bar{B} \bar{C} \bar{D}$

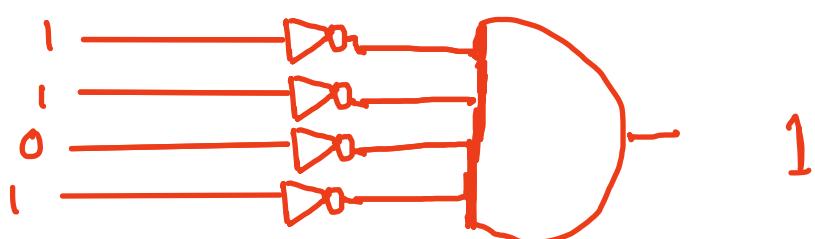

(iv) 11100

$A B C \bar{D} \bar{E}$

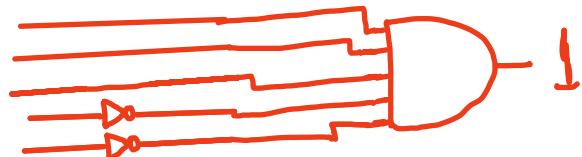


4. You wish to detect only the presence of the codes 1010, 1100, 0001, and 1011. An active-HIGH output is required to indicate their presence. Develop the minimum decoding logic with a single output that will indicate when any one of these codes is on the inputs. For any other code, the output must be LOW.

Sol:


$$X = A\bar{B}C\bar{D} + AB\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}CD$$

		AB	CD	00	01	11	10
		00	0	1	3	2	
		01	4	5	7	6	
		11	12	13	15	14	
		10	8	9	11	10	

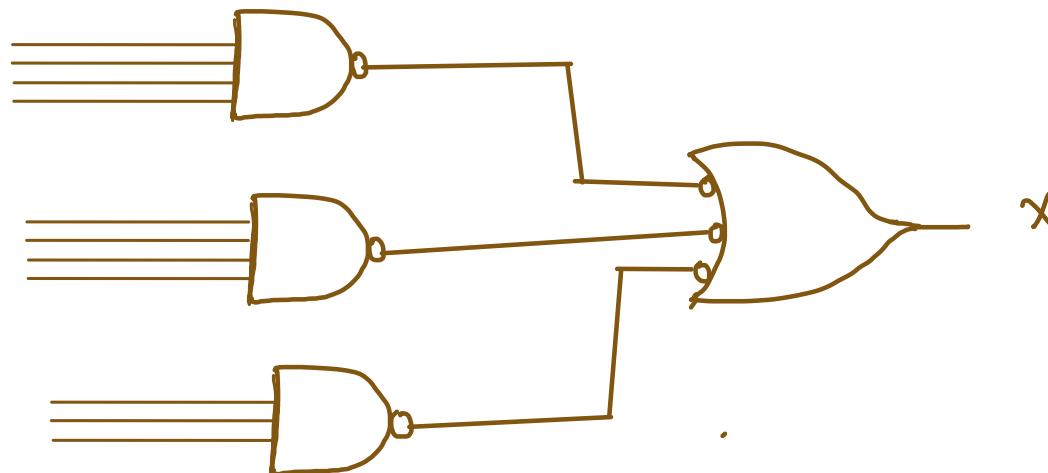
$$X = \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}C$$



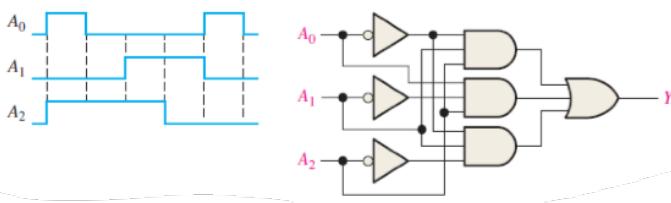
5. If the input waveforms are applied to the decoding logic as indicated in Figure 6-76, sketch the output waveform in proper relation to the inputs.




Sol:

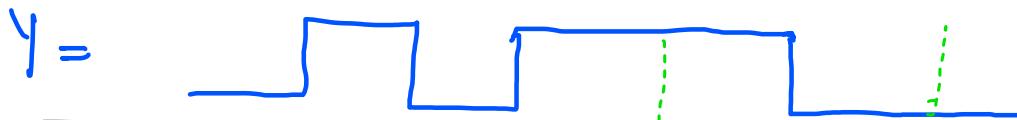

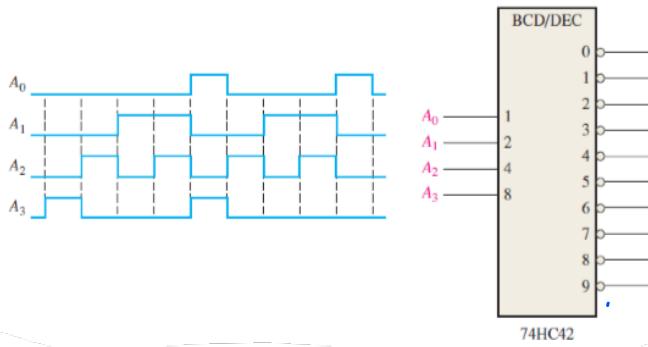
6. BCD numbers are applied sequentially to the BCD-to-decimal decoder in Figure 6-77. Draw a timing diagram, showing each output in the proper relationship with the others and with the inputs.



Sol:

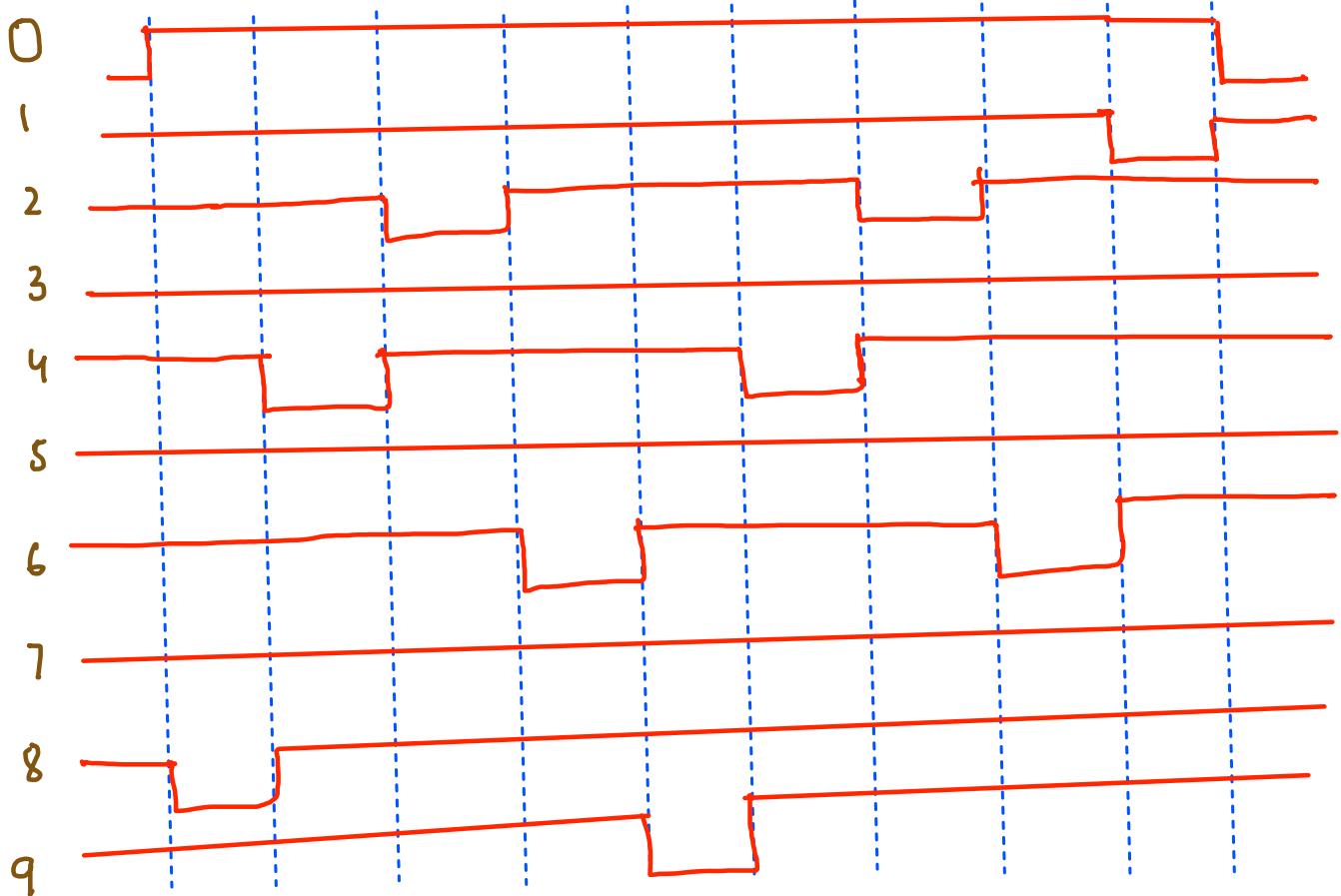

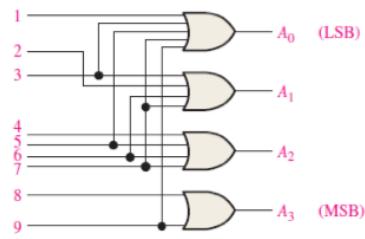7. For the decimal-to-BCD encoder logic of Figure, assume that the 9 input and the 3 input are both HIGH. What is the output code? Is it a valid BCD (8421) code?




Solution :

BCD (8421) is not valid

Reason being that when 9 (1001) and 3 (0011) are high, answer will be 13 (1101).

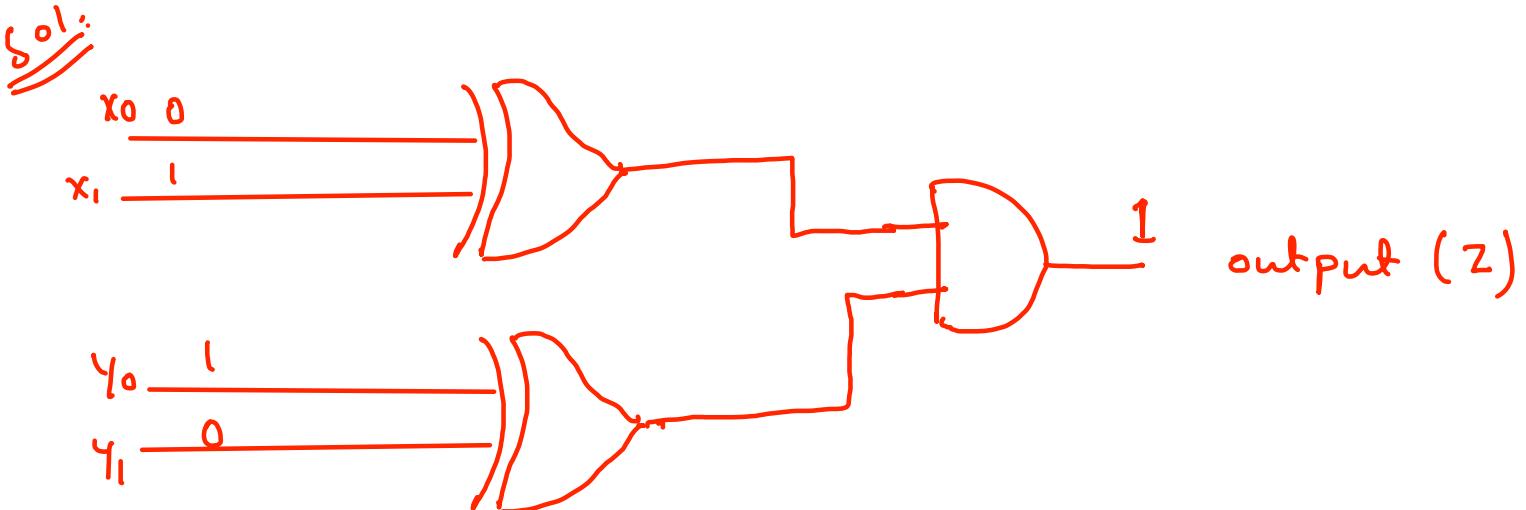8. The notation $x_1 x_0$ represents a two-bit binary number that can have any value (00, 01, 10, 11); for example, when $x_1 = 1$, $x_0 = 0$, the binary number is 10, and so on. Similarly, y_1 and y_0 represent another two-bit binary number. Design a logic circuit, using x_1, x_0, y_1 , and y_0 inputs, whose output will be HIGH only when the two binary numbers $x_1 x_0$ and $y_1 y_0$ are opposite.





9. Write the function table for a half subtractor (input A and B, output DIFF and CARRY). From the function table, design two logic circuits that will act as half subtractor.

Solution:

Truth table:


A	B	Diff	Carry
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

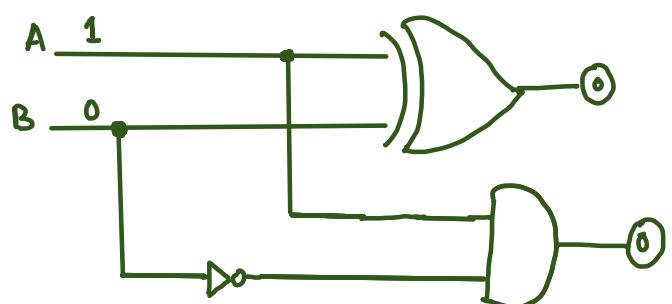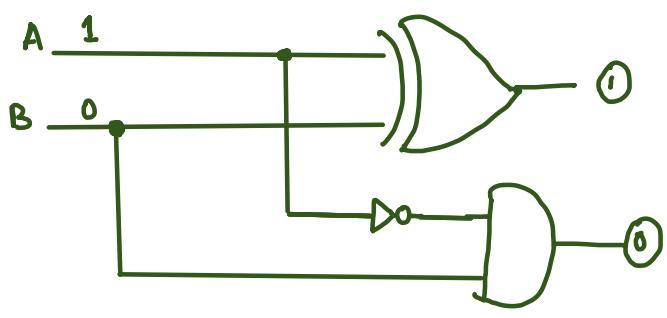


10. Derive an expression for a 2-bit magnitude comparator using Table.

Solution:


A ₂	A ₁	B ₂	B ₁	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

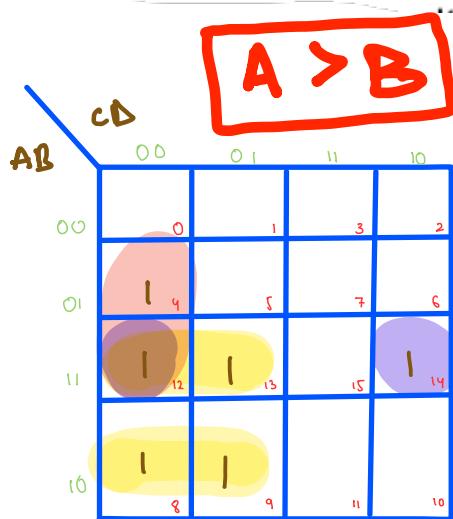
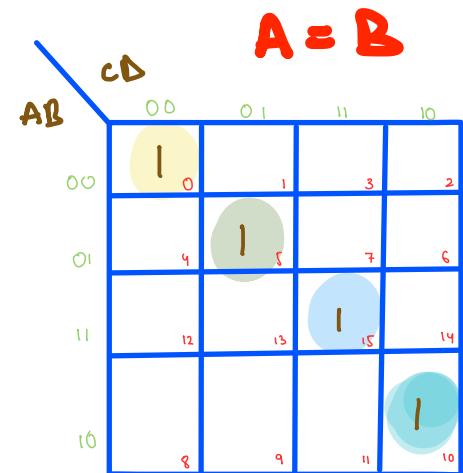
$$A > B = A_1 \bar{B}_1 + A_2 \bar{B}_1 \bar{B}_2 + A_1 A_2 \bar{B}_2$$


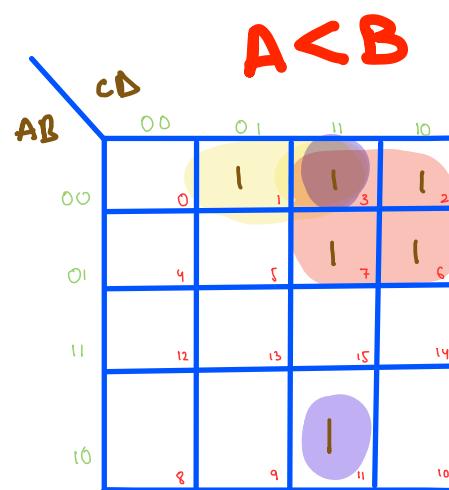
$$A = B = A_1 A_2 B_1 B_2 + A_1 A_2 B_1 \bar{B}_2 + A_1 \bar{A}_2 B_1 B_2 + A_1 \bar{A}_2 \bar{B}_1 \bar{B}_2$$



$$A < B = \bar{A}_1 \bar{A}_2 B_2 + \bar{A}_1 A_2 B_1 B_2 + \bar{A}_1 B_1$$

11. For the multiplexer in Figure 1, determine the output for the following input states: D₀ = 1, D₁ = 0, D₂ = 0, D₃ = 1,

- (a) S₀ = 0, S₁ = 1 (b) S₁ = 0, S₁ = 1 (c) S₀ = 1, S₁ = 0

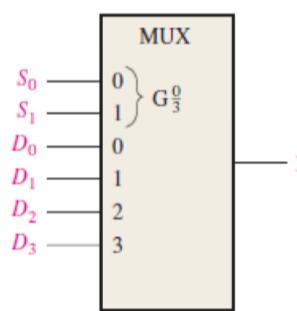


Figure 1

12. If the data-select inputs to the multiplexer in the above Figure 1 are sequenced as shown by the waveforms in Figure 2, determine the output waveform with the data inputs specified in Problem 3.

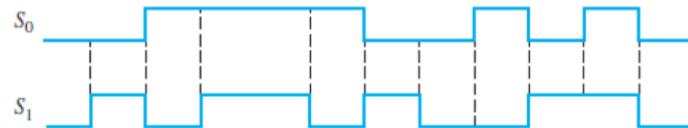


Figure 2

13. The waveforms in Figure 3 are observed on the inputs of a 74HC151 8-input multiplexer. Sketch the Y output waveform.

Sol Q11.


S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

a) S₀ > 0 S₁ = 1 ∴ D₂

b) S₀ = 1 S₁ = 1 ∴ D₃

c) S₀ = 1 S₁ = 0 ∴ D₁

Solution 12:

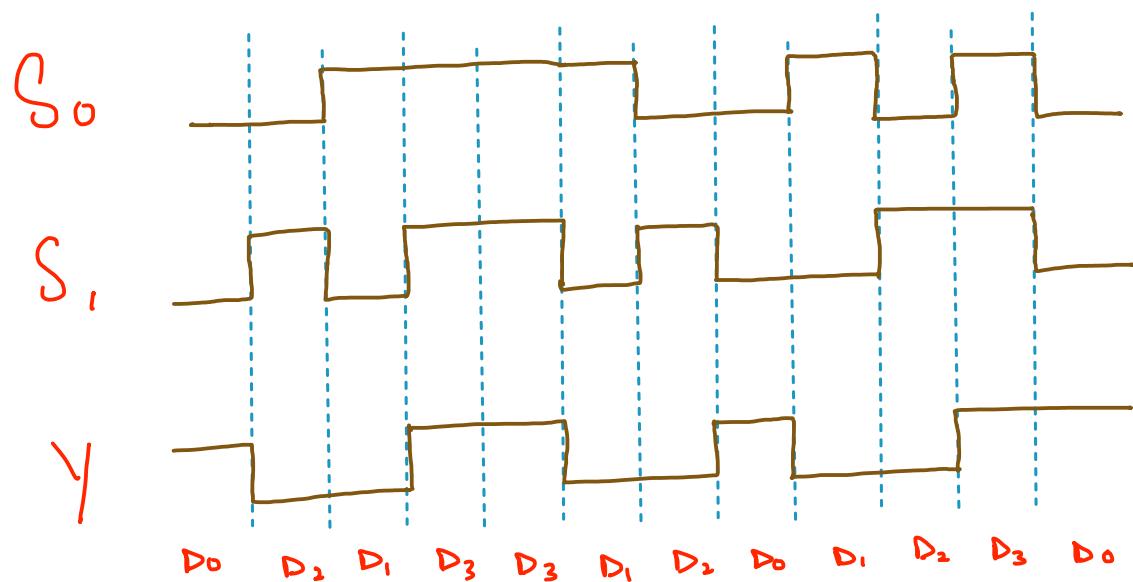


Solution 13:



18. Construct a 16 X 1 multiplexer with two 8x1 and one 2x1 multiplexers. Use block diagrams.


Solution :

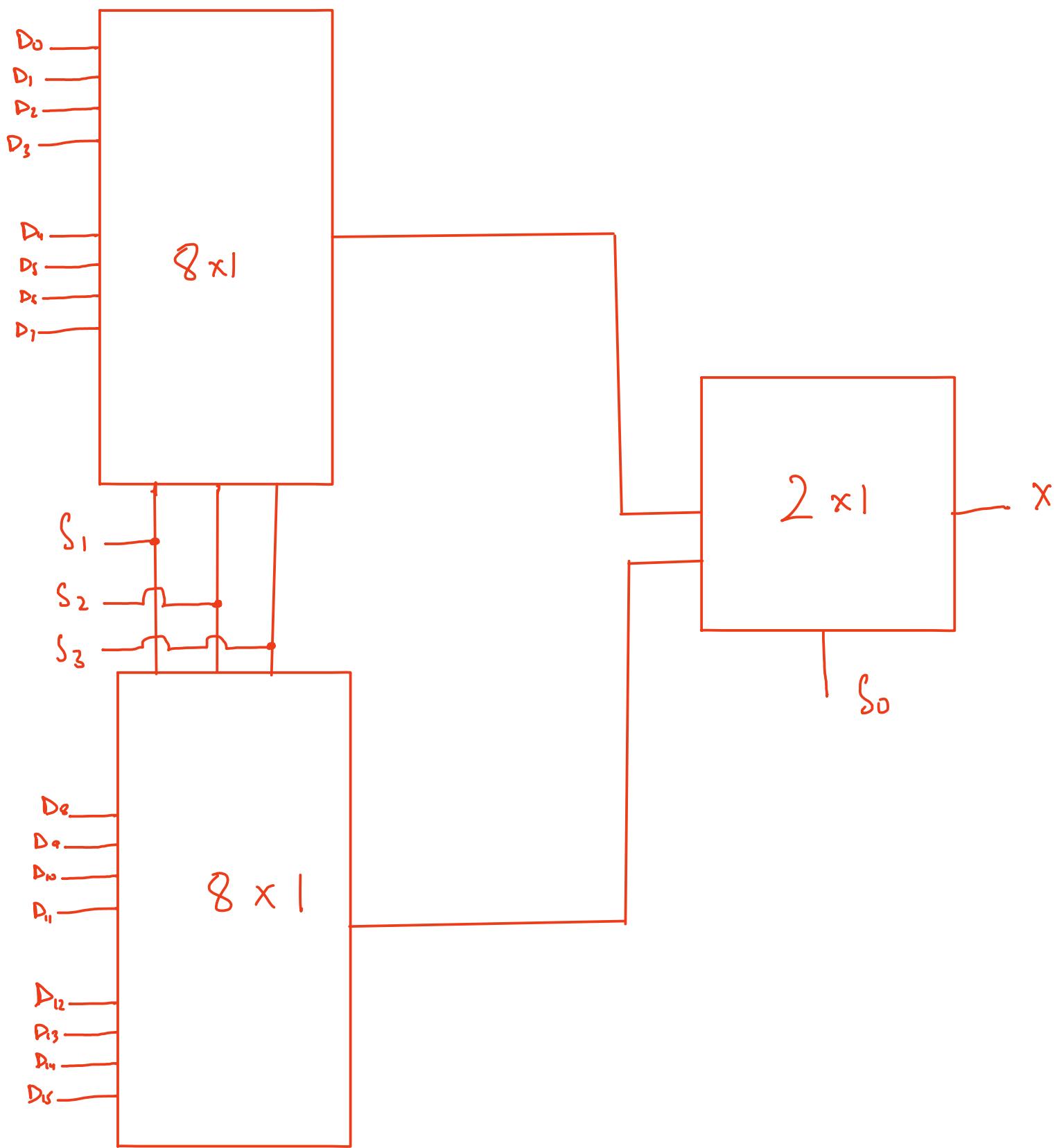

Date _____
M T W T F S S

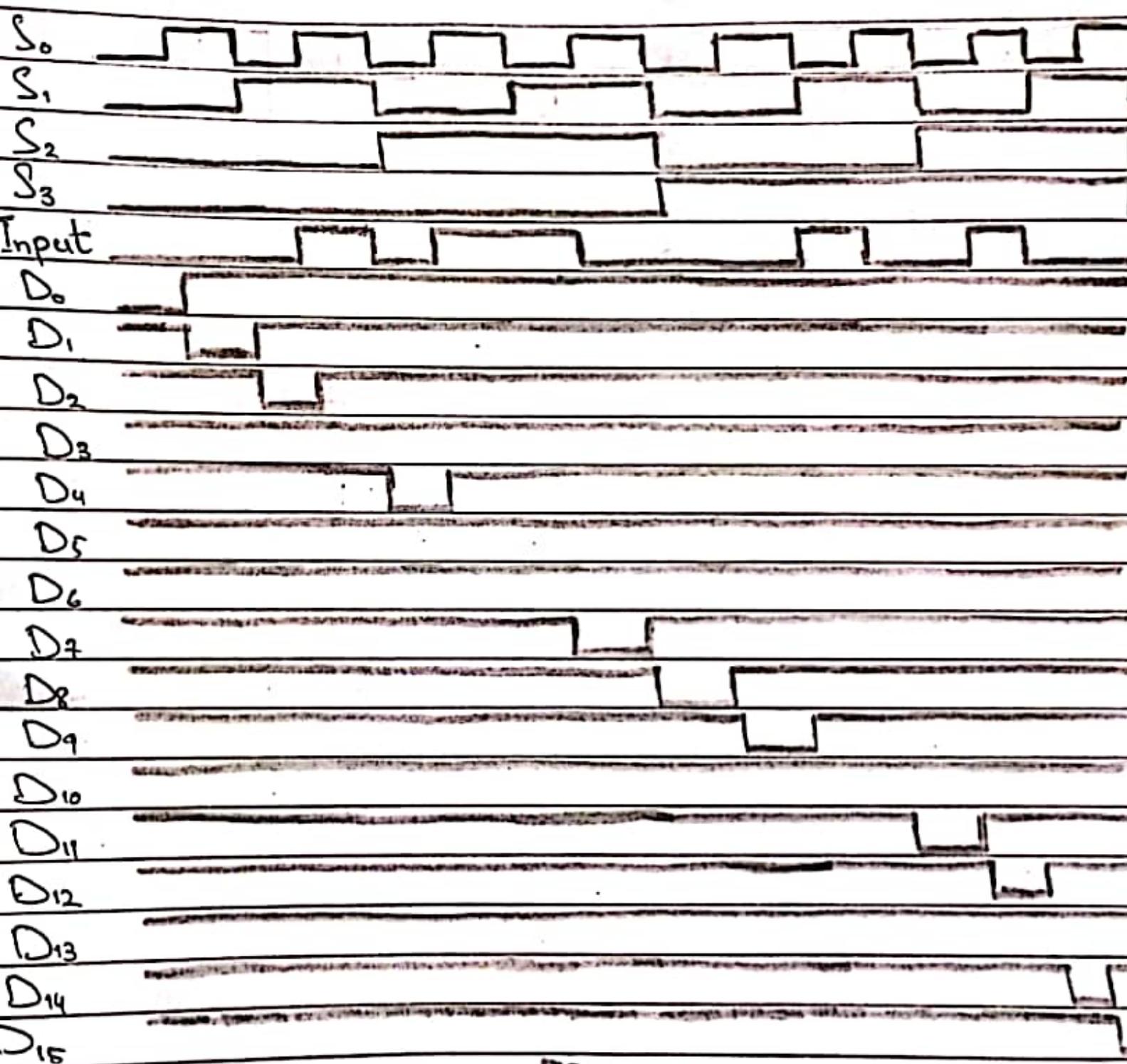Q14: Solution:

Data Input: 2468 : 0010010001101000 :
0001011000100100




Date _____

M	T	W	T	F	S	S
---	---	---	---	---	---	---

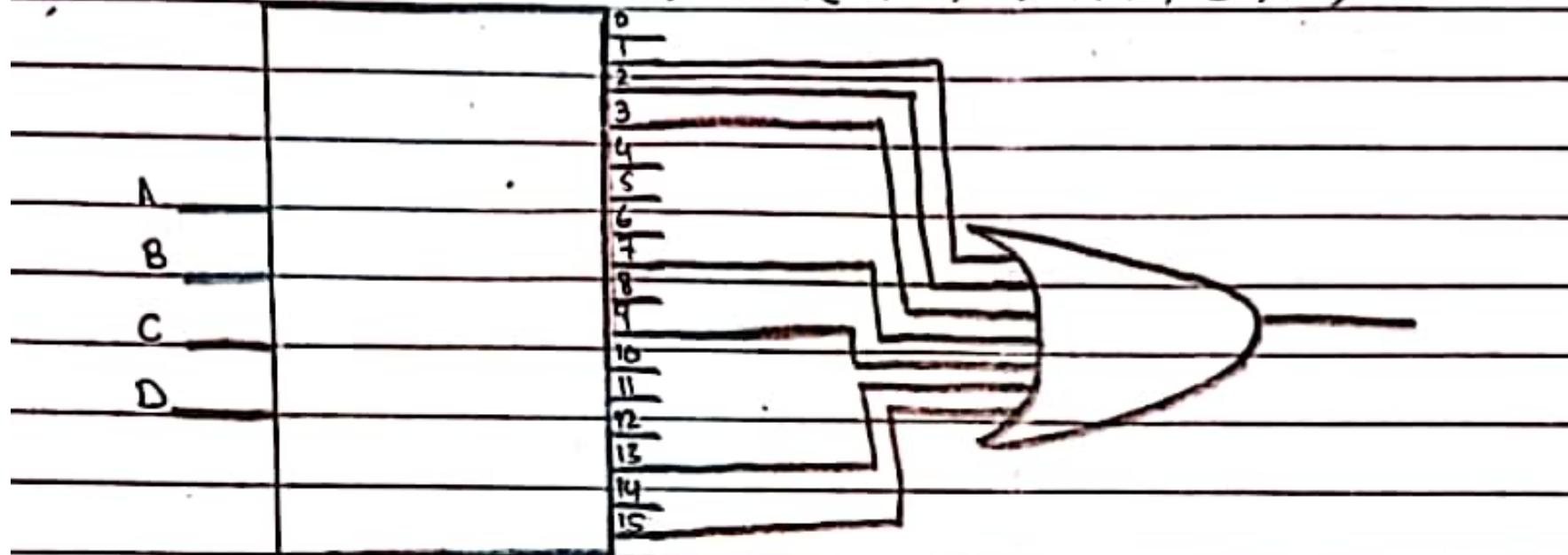Q15. Solutions

$$F(A, B, C, D) = \Sigma(1, 2, 3, 7, 9, 13, 15)$$



Date _____


M	T	W	T	F	S	S
---	---	---	---	---	---	---

Q16: Solution:

$$X(A_3, A_2, A_1, A_0) = \Sigma(2, 3, 4, 8, 9, 10, 11, 15)$$


	A ₃	A ₂	A ₁	A ₀	X	
0	0	0	0	0	0	X=0
1	0	0	0	1	0	
2	0	1	0	0	1	X=1
3	0	1	0	1	0	X=0
4	1	0	0	0	1	X=1
5	1	0	1	0	1	X=1
6	1	1	0	0	0	X=0
7	1	1	1	1	0	X=0

Date _____
 M T W T F S S

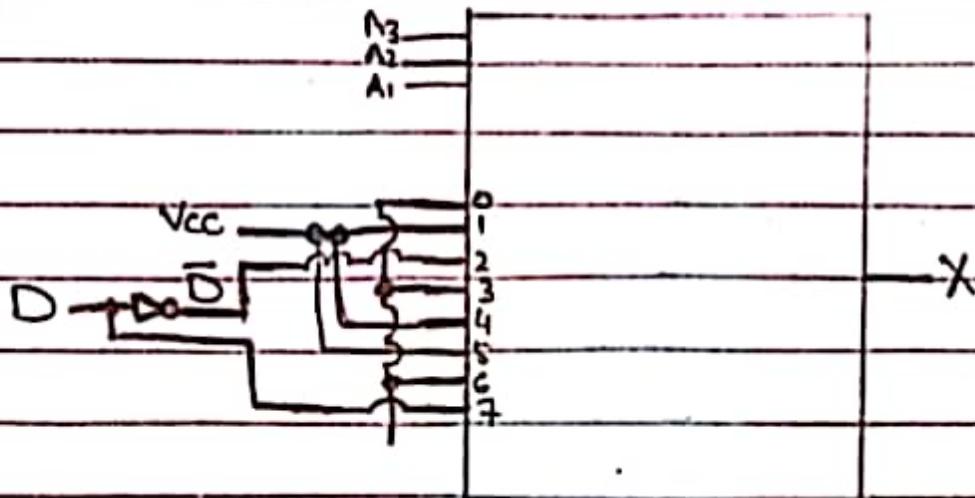

Q17.(a): Solution:

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

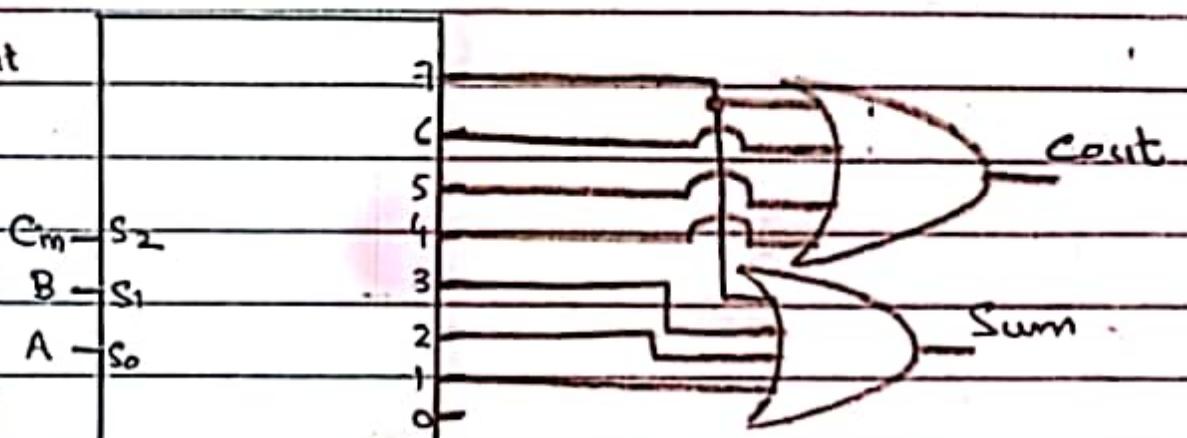

Date _____

M	T	W	T	F	S	S
---	---	---	---	---	---	---

Q17:(b): Solutions

A	B	Cin	Σ	Cout
0	0	0	0	0
0	0	1	1	0
1	0	0	1	0
1	0	1	0	1
2	1	0	0	1
2	1	0	0	1
3	1	1	0	0
3	1	1	1	1

