 



chap # 07

7-1 Latches

The S-R latch :



SET means $Q=1$
RESET means $Q=0$

 


Truth Table


\bar{S}	\bar{R}	Q	\bar{Q}
0	0	invalid	
0	1	1	0
1	0	0	1
1	1	no change	

S	R	Q	\bar{Q}
0	0	no change	
0	1	0	1
1	0	1	0
1	1	invalid	


Example 7-1

 

The Gated SR latch

 


logic diagram

 


logic symbol


Example 7-2

 

The Gated D Latch

 

logic diagram

 


logic symbol

Truth Table

E	D	Q
1	0	0
1	1	1

 if $E = 0 \rightarrow Q = \text{previous output}$




7-2 Flip Flops


- edge triggered flip flop changes state either at the positive edge or at the negative edge.

The D flip flop


Truth Table

clk	D	Q	\bar{Q}	
↑	0	0	1	reset
↑	1	1	0	set

 

 


The JK Flip Flop

 


Truth Table

CLK	J	K	Q	\bar{Q}	
↑	0	0	Q	\bar{Q}	no change
↑	0	1	0	1	reset
↑	1	0	1	0	set
↑	1	1	\bar{Q}	Q	toggle


 


Example 7-6 :

 


Asynchronous Preset and Clear Inputs

  - an active preset input makes the Q output "HIGH" (set)
- an active clear input makes the Q output "LOW" (reset)







7-4 Flip Flop Applications

Parallel Data Storage

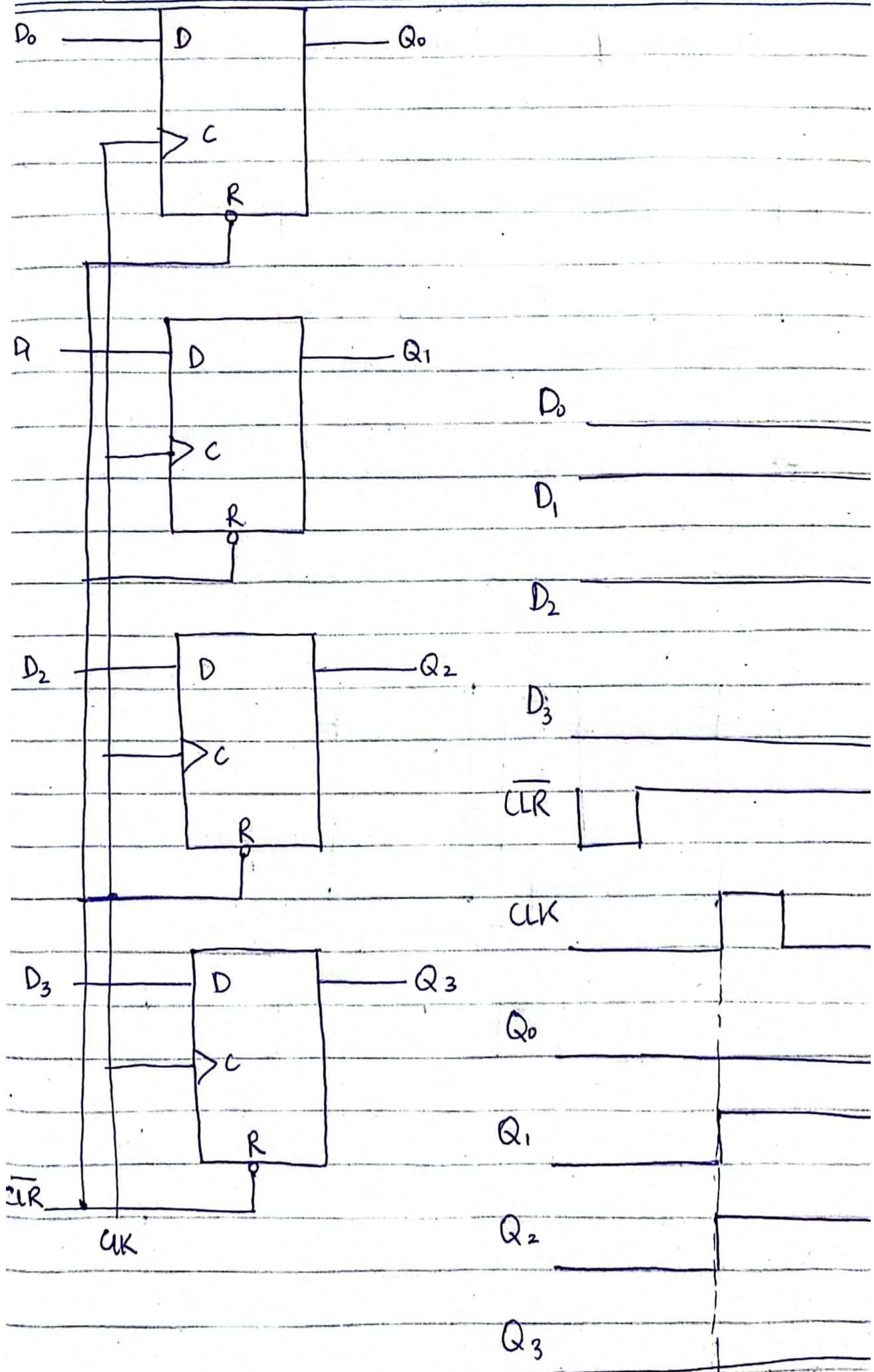

Frequency Division

    

Develop the f_{out} waveform.

