

NAND/NOR logic. (see lecture 15 and 16)

20. Implement the logic circuits in Figure 5–54 using only NAND gates.

21. Implement the logic circuit in Figure 5–58 using only NAND gates.

22. Repeat Problem 20 using only NOR gates.

23. Repeat Problem 21 using only NOR gates.


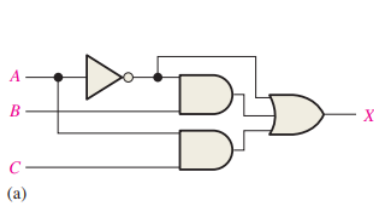


FIGURE 5–54

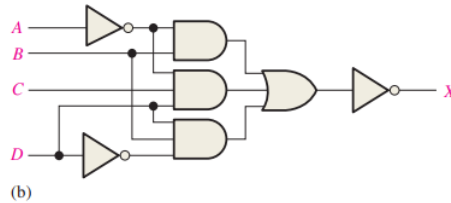

(b)


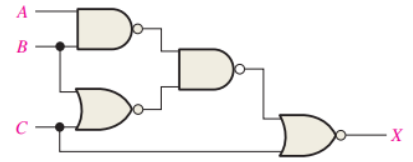


FIGURE 5–58

Remember, these circuits can be given to you in terms of logic expressions such as $X = \overline{(\overline{A} + \overline{B} + \overline{C})DE}$ & $X = \overline{\overline{A}\overline{B}\overline{C}} + (D + E)$

Adders & Comparators

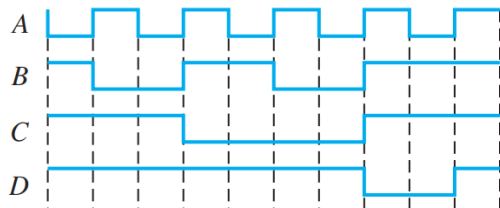Consider ABCD as a number, with D as LSB, and add the number to itself to write the outputs.



11. Each of the eight full-adders in an 8-bit parallel ripple carry adder exhibits the following propagation delay:

A to Σ and C_{out} :	20 ns
B to Σ and C_{out} :	20 ns
C_{in} to Σ :	30 ns
C_{in} to C_{out} :	25 ns

Determine the maximum total time for the addition of two 8-bit numbers.

Draw the comparator circuit that can compare two 8-bit numbers using 4-bit comparator circuit.

Practice questions for Mux/DeMux and Decoder/Encoders are enough from the assignment.