

110 100 0100

0110 1100 1000

0110 0000 1000

1000 1
0001
0000

1001
0110
1101

0110 1100 1000

0110

1011
1101

$\therefore (10)_2 = 10$

b):-

0	0	0	0	0		1	1	0	0	0
0	0	0	0	1		1	1	0	1	1
0	0	0	1	0		1	1	1	0	0
0	0	0	1	1		1	1	1	0	1
0	0	1	0	0		1	1	1	1	0
0	0	1	0	1		1	1	1	1	1
0	0	1	1	0		—				
0	0	1	1	1		—				
0	1	0	0	0		1	1	0	1	1
0	1	0	0	1		↓				
0	1	0	1	0		10110				
0	1	0	1	1						
0	1	1	0	0		11100				
0	1	1	0	1		↓				
0	1	1	1	0		10010				
0	1	1	1	1						
1	0	0	0	0		11101				
1	0	0	0	1		↓				
1	0	0	1	1		10011				
1	0	0	1	0						
1	0	0	1	1		11110				
1	0	1	0	0		↓				
1	0	1	0	1		10001				
1	0	1	1	0						
1	0	1	1	1		11111				
1	0	1	1	1		↓				
1	0	0	0	0		00000				
1	1	0	0	0						
1	1	0	0	1						

a(a) CD

AB	00	01	11	10
00	1			1
01	1	1		1
11		1	1	
10	1			1

$$\bar{B}\bar{C}\bar{D} + \bar{A}\bar{C}\bar{D} + B\bar{C}D + ABD + \bar{B}C\bar{D} + \bar{A}C\bar{D}$$

b):-


c):-

i):-

Assuming

A B C D
MSB ← LSB

AB	CD	00	01	11	10
00		1	1	1	1
01		1	1		1
11					
10					

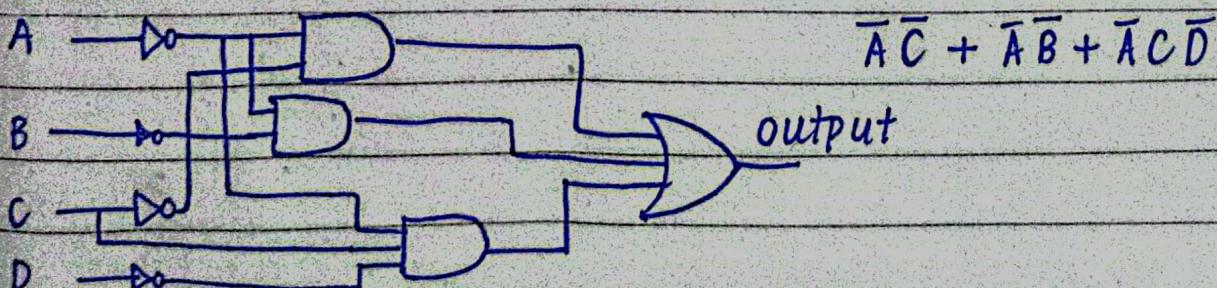


ii) :-

assuming


A B C D
msb ← LSB

AB	CD
00	1
01	1
11	1
10	1

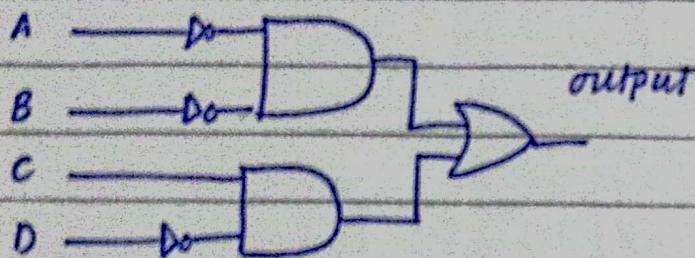


$$\bar{A}\bar{B} + C\bar{D}$$

Q3 (a) :-

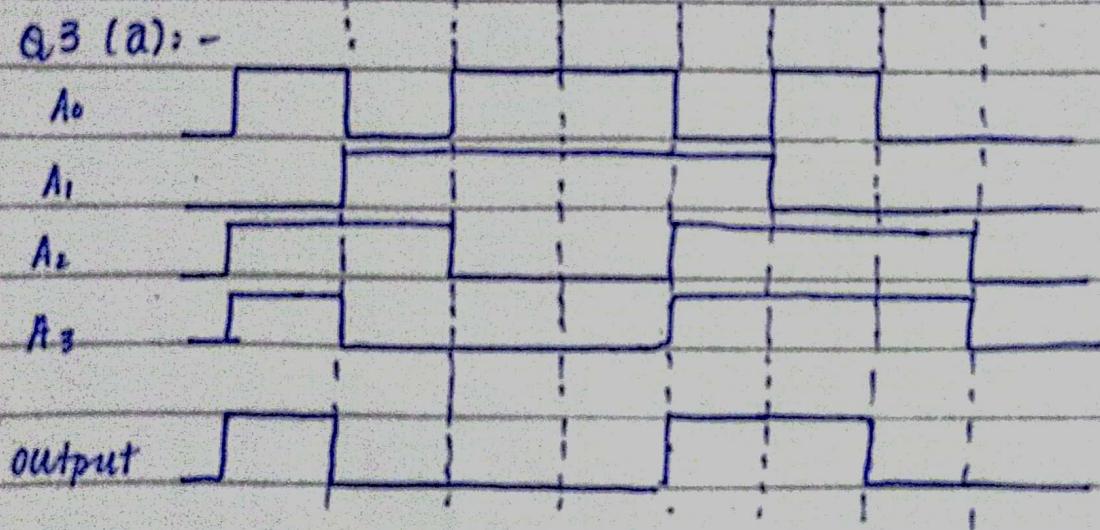

b) :-

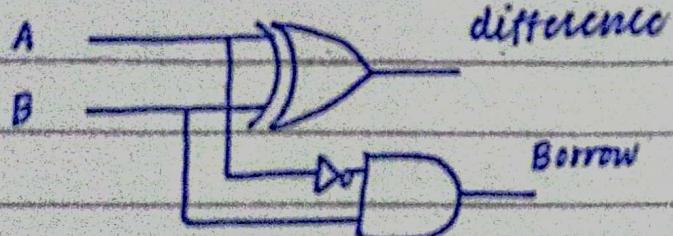


c) :-

$$X(A_3, A_2, A_1, A_0) = \Sigma(0, 1, 2, 5, 7, 10, 12)$$

		AIAO				
		00	01	11	10	
A3 A2		00	1	1	1	1
01		01		1		
11		11	1			
10		10			1	


Analysis of A0 with respect to A3, A2, A1

Vcc / +5V

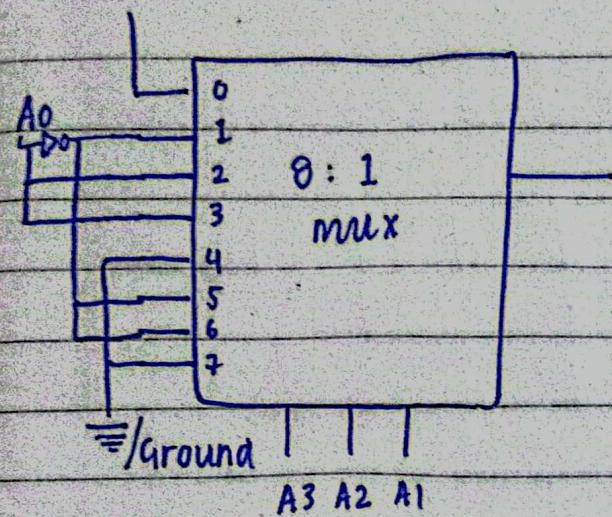

A3	A2	A1	output
0	0	0	1 always
0	0	1	A0
0	1	0	A0
0	1	1	A0
1	0	0	0
1	0	1	A0
1	1	0	A0
1	1	1	0

d) :-

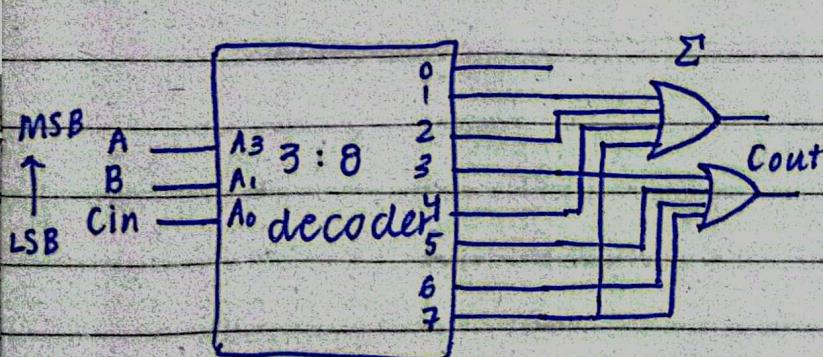


A	B	Cin	Σ	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

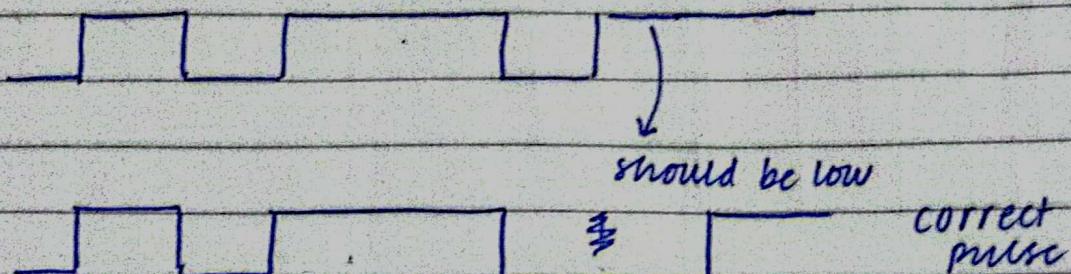Q4


a):-

output corresponding to the sixth clock pulse is faulty




b):-

Assuming D given zero initially

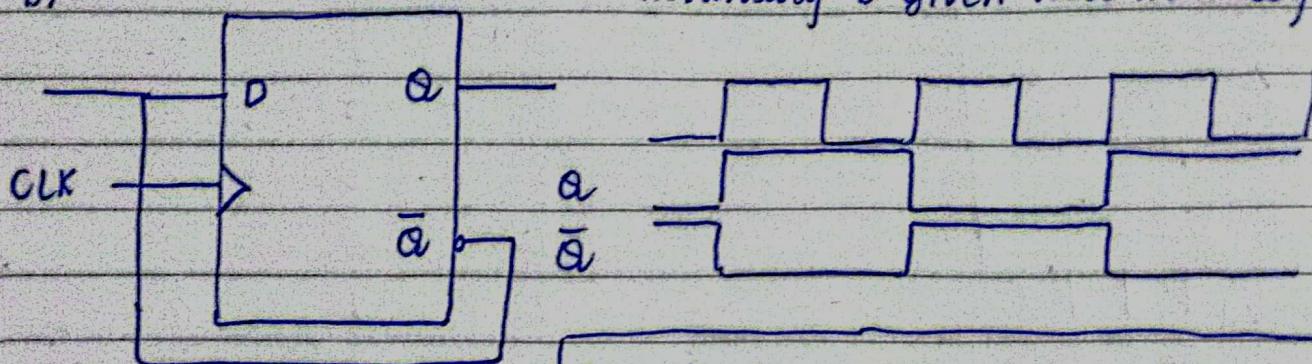


c):-

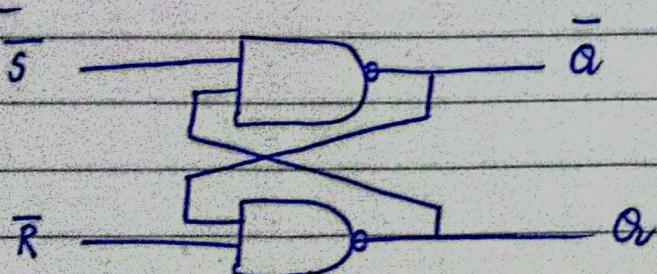


\bar{S}	\bar{R}	Q	\bar{Q}
0	1	1	0
1	0	0	1
1	1	Q	\bar{Q}
X	X	invalid	invalid


Assuming Q to be low initially

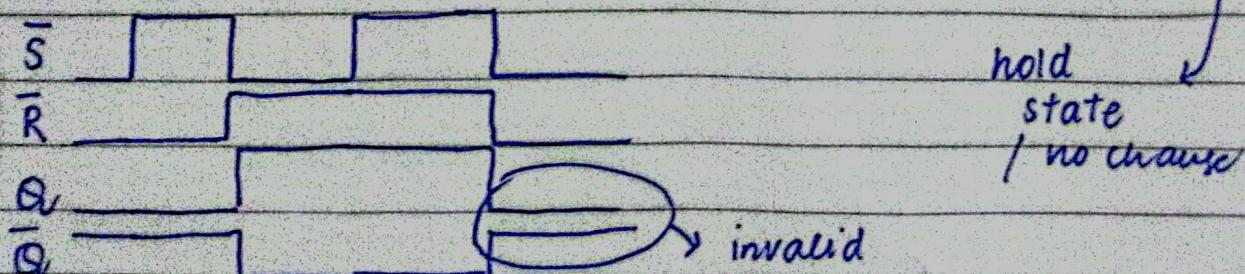

Q4(d)

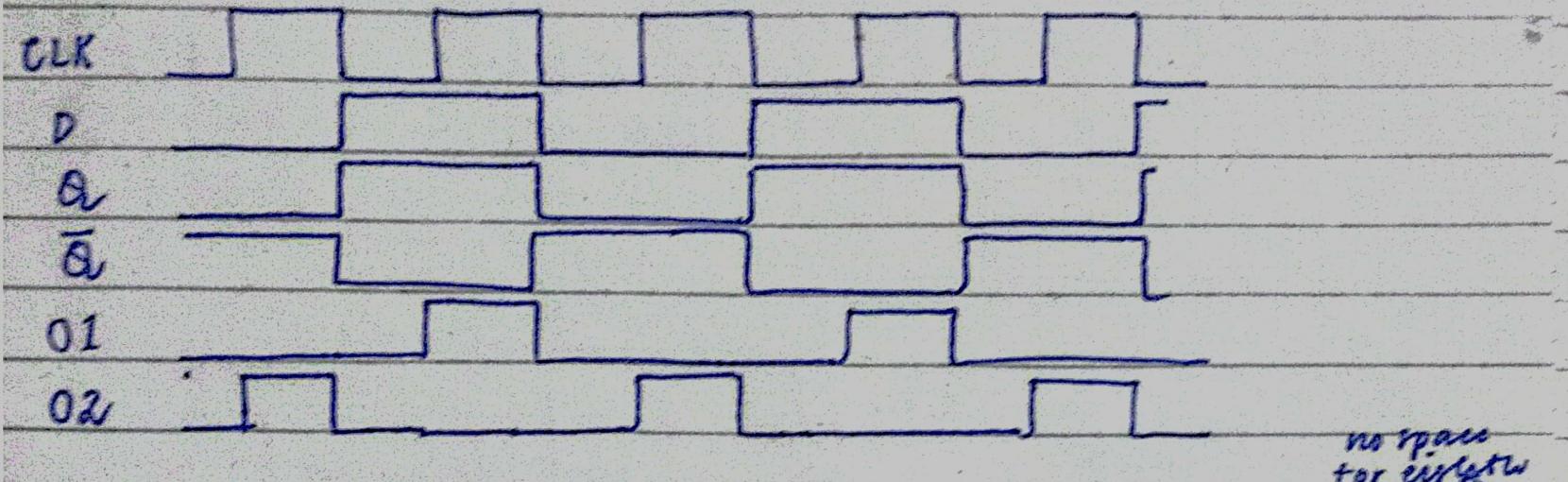


(e)

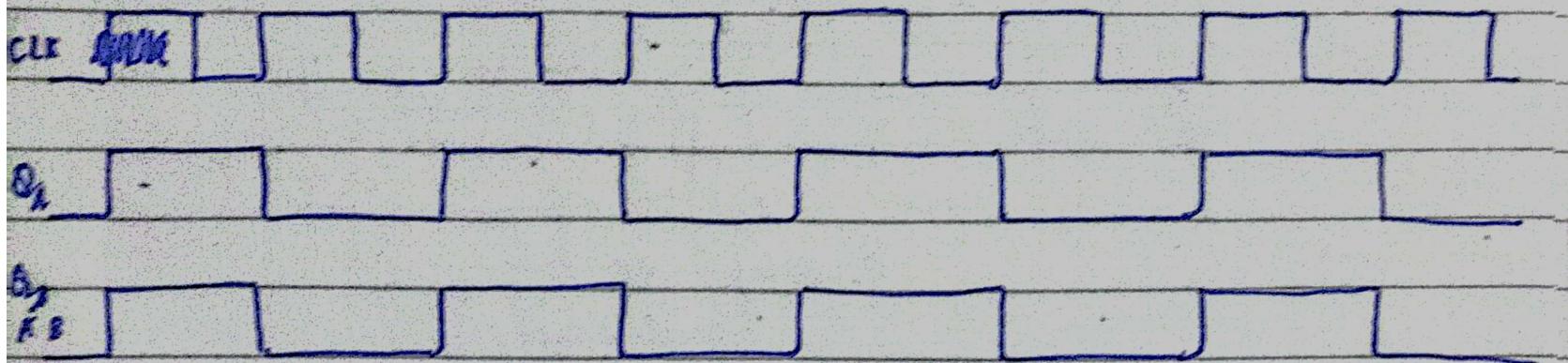

Vcc / +5V

Q15 :-

a) :-

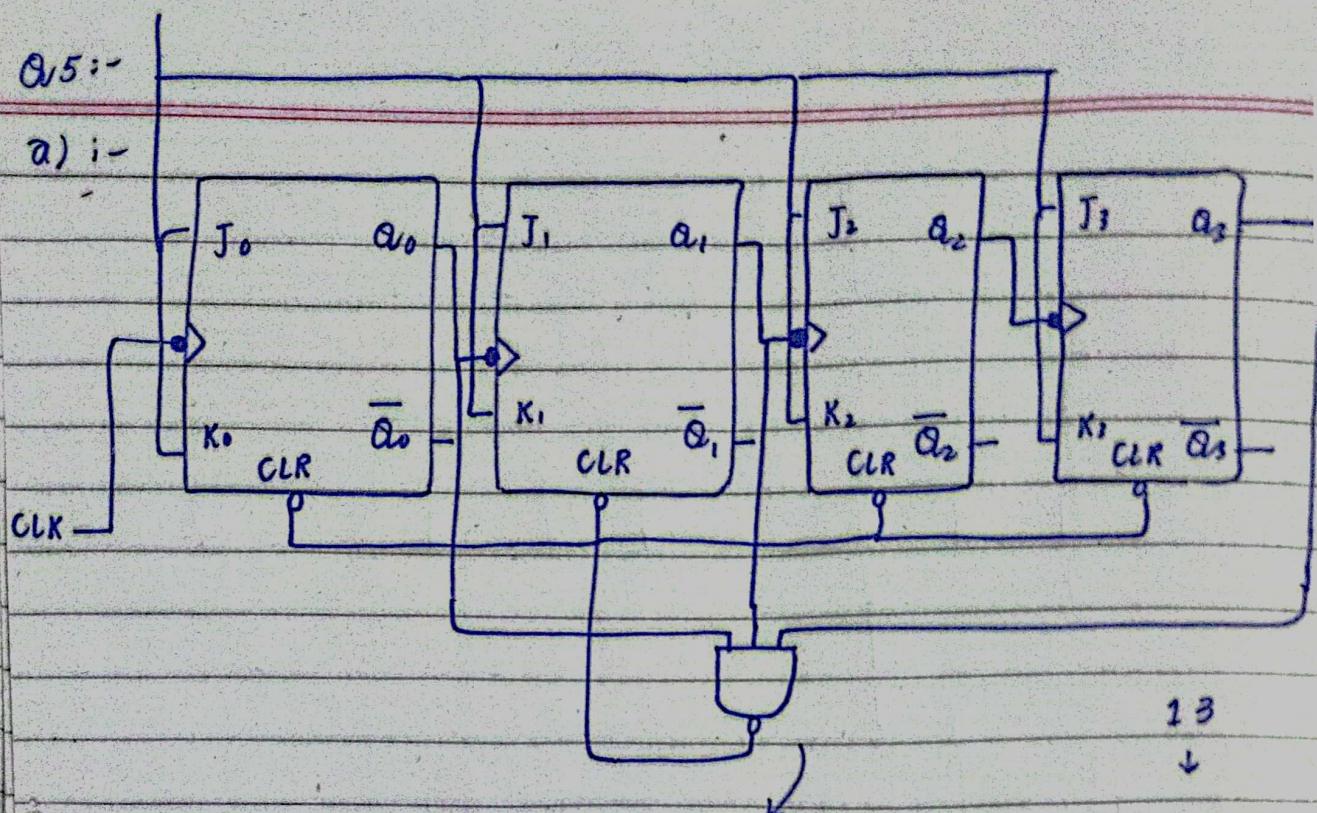

13

↓
1101

since no other
state has

1's on


$Q_0, Q_1, Q_2,$

and Q_3

is already 0

(ii) :-

Vcc / +5V

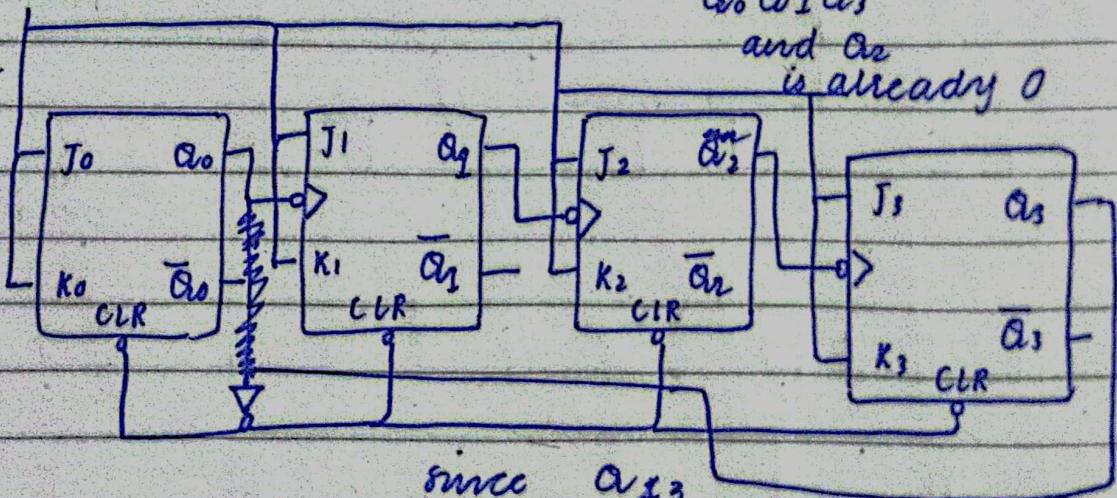


since Q_{13}

is only 1 on 8

and others

are already 0

1 up ($Y=0$)

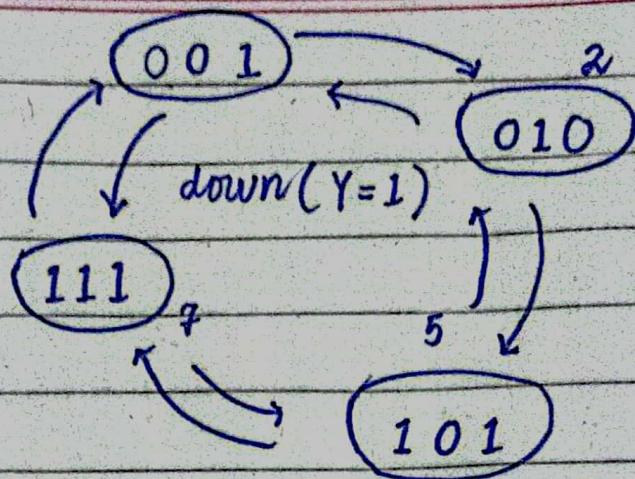

J-K Excitation table :-

J

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Circuit Excitation Table

Y	Q_3	Q_2	Q_1	Q_3^*	Q_2^*	Q_1^*	J_3	J_2	J_1	K_3	K_2	K_1
0	0	0	1	0	1	0	0	1	X	X	X	1
0	0	1	0	1	0	1	1	X	1	X	1	X
0	1	0	1	1	1	1	X	1	X	0	X	0
0	1	1	1	0	0	1	X	X	X	1	1	0
1	0	0	1	1	1	1	1	1	X	X	X	0
1	0	1	0	0	0	1	0	X	1	X	1	X
1	1	0	1	0	1	0	X	1	X	1	X	1
1	1	1	1	1	0	1	X	X	X	0	1	0

$Q_2 Q_1$		J ₃				$Q_2 Q_1$		J ₂				$Q_2 Q_1$		J ₁			
$Y Q_3$	00	00	01	11	10	$Y Q_3$	00	00	01	11	10	$Y Q_3$	00	00	01	11	10
00	X	0	X	1		00	X	1	X	X		00	X	X	X	1	
01	X	X	X	X		01	X	1	X	X		01	X	X	X	X	
11	X	X	X	X		11	X	1	X	X		11	X	X	X	X	
10	X	1	X	0		10	X	1	X	X		10	X	X	X	1	

$Q_2 Q_1$		K ₃				$Q_2 Q_1$		K ₂				$Q_2 Q_1$		K ₁			
$Y Q_3$	00	01	11	10	$Y Q_3$	00	01	11	10	$Y Q_3$	00	00	01	11	10		
00	X	X	X	X		00	X	X	X	1		00	X	1	X	X	
01	X	0	1	X		01	X	X	1	X		01	X	0	0	X	
11	X	1	0	X		11	X	X	1	X		11	X	1	0	X	
10	X	X	X	X		10	X	X	X	1		10	X	0	X	X	

$$J_3 = \overline{Q_2} + Q_1 \quad K_3 = \overline{Q_2} + Q_1$$

$$J_2 = 1$$

$$J_1 = 1$$

$$K_2 = 1$$

$$K_1 = \overline{Y Q_3} + Y Q_3 \overline{Q_2}$$

