
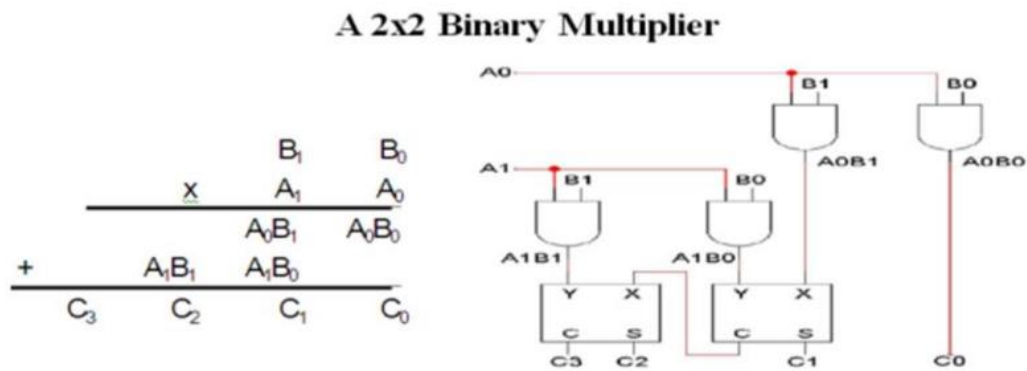


2x2 Binary Multiplier:

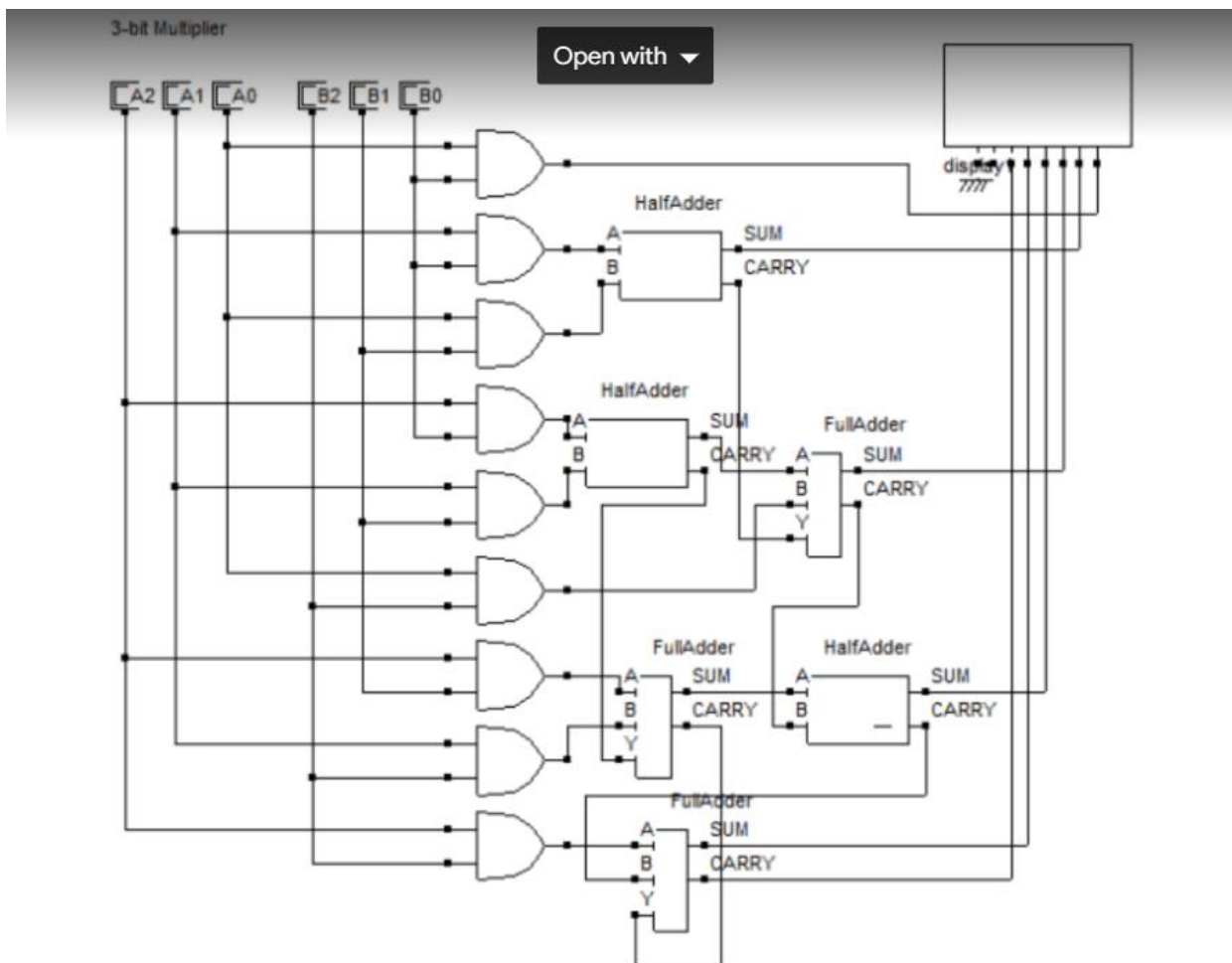

3x3 Binary Multiplier:




Half Adder:




Truth Table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


Full Adder:

 



TRUTH TABLE

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Half Subtractor:

Circuit Diagram:

  

A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Subtractor:

 

Minuend (A)	Subtrahend (B)	Borrow In (B _{in})	Difference (D)	Borrow Out (B _o)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



one-bit comparator:

Function Table:

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

H= Logic High, L= Logic Low

Connection Diagram:

  

74148 (8 x 3) Octal to Binary Priority Encoder:

 


Figure 2. Functional block diagram 74LS148

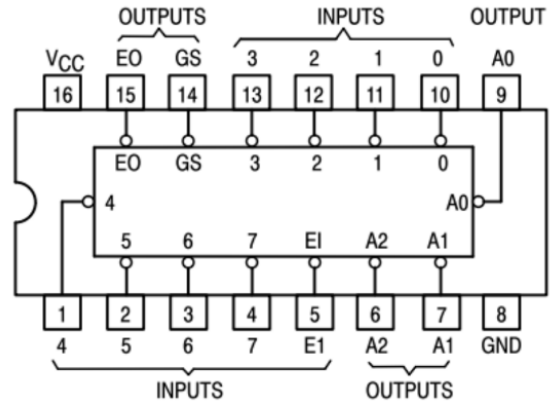


Figure 3. 8to3 Priority Encoding

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	Y ₂	Y ₁	Y ₀
1	0	0	0	0	0	0	0	0	0	0
x	1	0	0	0	0	0	0	0	0	1
x	x	1	0	0	0	0	0	0	1	0
x	x	x	1	0	0	0	0	0	1	1
x	x	x	x	1	0	0	0	1	0	0
x	x	x	x	x	1	0	0	1	0	1
x	x	x	x	x	x	1	0	1	1	0
x	x	x	x	x	x	x	1	1	1	1

Decimal to BCD Priority Encoder (74147):



 


Figure 5. Functional block diagram 74LS147

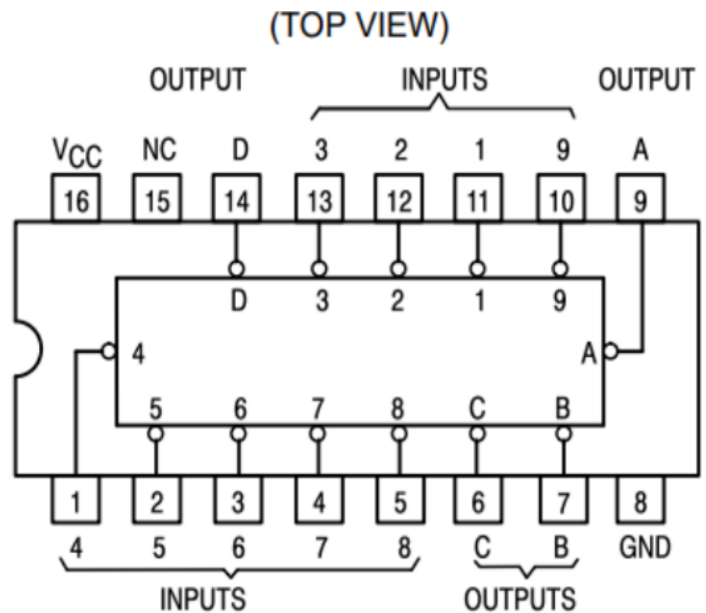

Decimal Inputs									BCD Outputs			
D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉	Y ₃	Y ₂	Y ₁	Y ₀
1	1	1	1	1	1	1	1	1	1	1	1	1
×	×	×	×	×	×	×	×	0	0	1	1	0
×	×	×	×	×	×	×	0	1	0	1	1	1
×	×	×	×	×	×	0	1	1	1	0	0	0
×	×	×	×	×	0	1	1	1	1	0	0	1
×	×	×	×	0	1	1	1	1	1	0	1	0
×	×	×	0	1	1	1	1	1	1	0	1	1
×	×	0	1	1	1	1	1	1	1	1	0	0
×	0	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	0

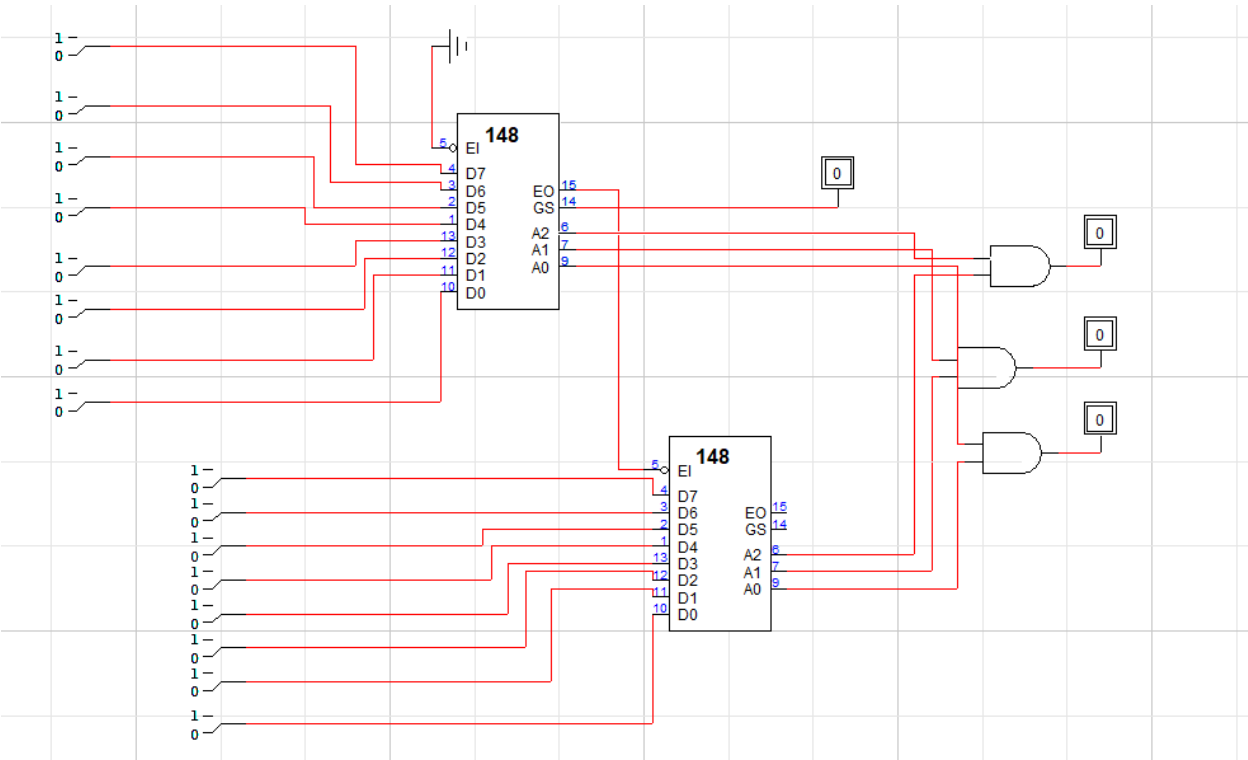16 bit Octal to Binary Priority Encoder using 74148 IC.:



Implementation of 3-8-line Decoder using IC 74LS138:

 


Fig 1. Pin Configuration

 


Fig 2. Logic Symbol

$A_0 - A_2$	Input Bits
G_{2A}', G_{2B}'	Enable (Active LOW) Inputs
G_1	Enable (Active HIGH) Inputs
$Y_0' - Y_7'$	Active LOW Outputs

Implementation of BCD to Seven Segment Decoder using IC 74LS47:

 


Fig 3. Pin Configuration

 


Fig 4. Logic Symbol

$A_0 - A_3$	BCD Inputs
RBI'	Ripple Blanking Input (Active LOW)
LT'	Lamp Test Input (Active LOW)
BI'/RBO'	Blanking Input or Ripple Blanking Output (Active LOW)
$a' - g'$	Active LOW Outputs

8x1 Multiplexer:

 


Fig 1. Pin Configuration

 


Fig 2. Logic Symbol

PIN Description:

S0–S2	Select Inputs
E'	Enable (Active LOW)
Input I0–I7	Multiplexer Inputs
Z	Multiplexer Output
Z'	Complementary Multiplexer Output

SR Latch Using NOR Gate:

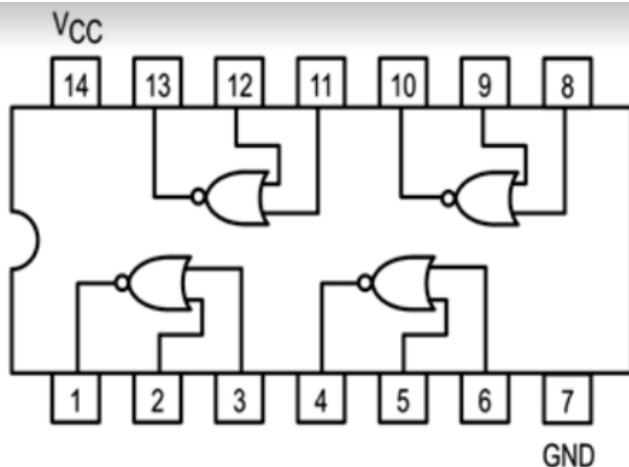


Figure. IC 74LS02 Pin Configuration

 


Figure. SR Latch Logic Diagram

Function Table of SR Latch

Inputs		Outputs		Comments
S	R	Q	Q'	
0	0			
0	1	0	1	
1	0	1	0	
1	1	1	1	

D Latch:

 


Figure. D Latch Logic Diagram



Function Table of D Latch

Inputs				Outputs		Comments
S	R	E	D	Q	Q'	
		0	0			
		0	1			
		1	0	0	1	
		1	1	1	0	

Edge Triggered D Flip-Flop:

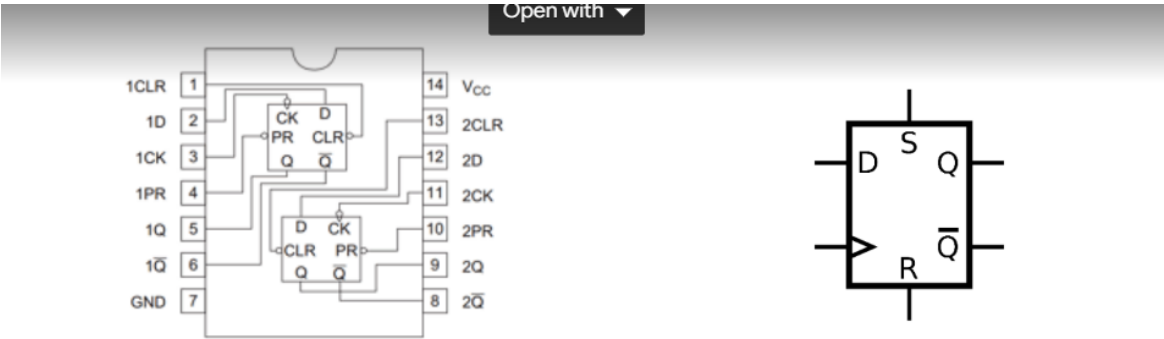


Figure. IC 74LS74 Pin Configuration

Figure. Graphic symbol D flip-flop

Function Table of D Flip-Flop

Inputs				Outputs		Comments
D	CLK	Preset	Clear	Q	Q'	

JK Flip-Flop:

 


Figure. Graphic symbol JK Flip-Flop

Truth Table			
J	K	CLK	Q
0	0	↑	Q ₀ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Q ₀ (toggles)

Figure. JK Flip-Flop Truth Table

Dual JK Flip Flop 74LS73

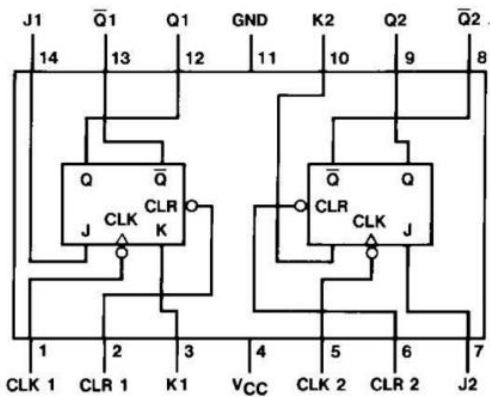


Figure. IC 74LS73 Pin Configuration

CLR	CLK	J	K	Q	Q̄
L	X	X	X	L	H
H	↓	L	H	L	H
H	↓	H	L	H	L
H	↓	L	L	Retains previous state	
H	↓	H	H	Toggle	

Figure. Dual JK Flip-Flop Truth Table

