

INFORMATION TECHNOLOGY UNIVERSITY, LAHORE, PAKISTAN

Department of Computer Engineering  
Digital Logic Design (CE-201T)

Final Exam, Fall 2022

Time Allowed: 3 Hours

December, 2022

Marks: 100

Name: Zainab Bashir

Roll Number: BSCE21013

Instructions:

- This Midterm Exam will access your CLOs as per OBE.
- Use only BLACK or BLUE ink pen.
- Write down your roll number on each page at the top in the given space.
- Use only the given space to solve the problem and write down your answers.
- Use pencils to draw the circuit diagrams.
- Manage your allotted time with care as you have limited time to solve the paper.
- It is a closed book/closed notes exam; so you must not have any material with you during this exam.
- If any student is found cheating or helping any other student, his/her exam will be cancelled and the case will be forwarded to Disciplinary Committee for further action.


CLOs

1. Apply the concept of different number systems and representations, to perform number system conversions and arithmetic operations.
2. Apply the concepts of Boolean algebra and logic simplification to realize simplified designs of combinational and sequential circuits.
3. Demonstrate the design of sequential circuits from their respective finite state machine representations.

Marks Distribution

Q. No.	CLO	Marks	Marks Obtained
1	1	20	20
2	2	20	20
3	2	20	20
4	3	20	18
5	3	20	19
6	3	20	20
7	3	20	19
Total	-	140	136

Instructor's Name: Aftab Alam

Signature: 

## 1. [CLO1]

- (a) Convert the hexadecimal number  $(4AC)_{16}$  into binary, octal and decimal. Show your work. 6/ [6]

$$\begin{array}{ccc|ccc|l}
 4 & A & C & 0100 & 1010 & 1100 & (4 \times 16^2) + (10 \times 16^1) + (12 \times 16^0) \\
 \downarrow & \downarrow & \downarrow & 2 & 2 & 5 & 4 \\
 0100 & 1010 & 1100 & & & & = 1196
 \end{array}$$

A 10  
B 11  
C 12  
D 13  
E 14  
F 15

$$(4AC)_{16} = (010010101100)_2 = (2254)_8 = (1196)_{10}$$

- (b) What is the decimal equivalent of the binary number 10010110 if it has been encoded as 6/ [6]

i. an 8-bit unsigned number.

$$(10010110)_2 = (150)_{10}$$

ii. an 8-bit signed number (represented in 2's complement form).

$$\begin{array}{r}
 10010110 \\
 01101001 \\
 \hline
 11111111 \\
 +1 \\
 \hline
 01101010 = 106
 \end{array}$$

128 64 32 16 8 4 2 1

$$128 - 127$$

$$= (-106)_{10}$$

iii. a BCD number

$$\begin{array}{cc}
 1001 & 0110 \\
 \downarrow & \downarrow \\
 9 & 6
 \end{array}$$

= 96

- (c) A digital system uses even parity for error detection. What parity bit will be appended to the 7-bit number 1101001 using this scheme? 2/ [2]

$$1101001$$

$$\text{parity bit} = 0$$

$$\text{8-bit num} = 01101001$$

(d) Show the addition of the two hexadecimal numbers 3999 and A803.

$$\begin{array}{r} 3999 \\ + A803 \\ \hline E19C \end{array}$$

14745

43011

57756

E19C

411

111111

101

1111

rough.

(e) The following arithmetic operation is correct in at least one number system. Determine the possible radices of the numbers in each operation.

i.  $\sqrt{41} = 5$

ii.  $\frac{41}{3} = 13$

(i)  $\sqrt{41} = 5$

~~$(4r+1)^{1/2} = 5$~~

~~$4r+1 = 25$~~

$\Rightarrow \sqrt{4r+1} = 5$

$4r+1 = 5^2$

$4r+1-5^2=0$

$4r-24=0$

$r=6$

it is in

base 6 number system

$(4 \times 6) + 1 = 25$

$5 = 5$

(ii)  $(41) = (13 \times 3)$

$4 \times r + 1 = ((1 \times r) + 3)(3)$

$4r + 1 = (r+3)(3)$

$4r + 1 = 3r + 9$

$4r - 3r = 9 - 1$

$r=8$

it is in octal number system.



## 2. [CLO2]

- (a) Write down the function  $F$  (Figure 1(a)) in  $\Pi$  notation (Product of Maxterms form) and the function  $G$  (Figure 1(b)) in  $\Sigma$  notation (Sum of Minterms form). 10

 


Figure 1(a)

 


Figure 1(b)

$$F = (\overline{A}B) + (BC)$$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

~~F = \Sigma m(6)~~

$$F = \Pi M(6)$$

$$F = (\overline{A} + \overline{B} + C)$$

$$G = ((\overline{A}B)B)(\overline{C}B)$$

A	B	C	$\overline{A}B$	$(\overline{A}B)B$	$\overline{C}B$	G
0	0	0	1	0	1	0
0	0	1	1	0	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	0	0	1	0
1	0	1	0	0	0	0
1	1	0	0	1	1	1
1	1	1	0	1	0	1


$$G = \overline{A}B + CB \quad (\text{After simplification})$$

$$G = \Sigma m(2, 3, 7)$$

$$G = (\overline{A}B\overline{C}) + (\overline{A}BC) + (ABC)$$

- (b) Draw the truth table for the circuit shown in Figure 2 with  $x, y$  and  $z$  as the inputs and  $A$  and  $B$  as the outputs. Which device is implemented using MUXs in Figure 2? Justify. 10 [6+4]

Figure 2

 

$x$	$y$	$z$	$A$	$B$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The function implemented is a full adder with  $B$  as the sum and  $A$  as the carry out.

e.g.  $m(4) \downarrow$

$$\begin{array}{ccc|cc} x & y & z & & \\ 1 & 0 & 0 & & \\ \hline s = 1 & & & B = 1 & \\ c = 0 & & & A = 0 & \end{array}$$

$$\begin{array}{ccc|cc} x & y & z & & \\ 1 & 1 & 1 & & \\ \hline \text{sum} = 1 & & & B = 1 & \\ \text{cout} = 1 & & & A = 1 & \end{array}$$

## 3. [CLO2]


- (a) A BCD code is being transmitted to a remote receiver. The bits are  $w, x, y$  and  $z$  with  $w$  as the Most Significant Bit. Design a BCD error detector circuit at the receiver that examines the BCD code to see if it is a legal BCD code. Implement your circuit using 8 x 1 Multiplexer. 10/10

w	x	y	z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


$$F = wx + wy$$

The output alerts if the BCD code is illegal.

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	3
0	1	1	3
1	0	0	3
1	0	1	3
1	1	0	3
1	1	1	3

 

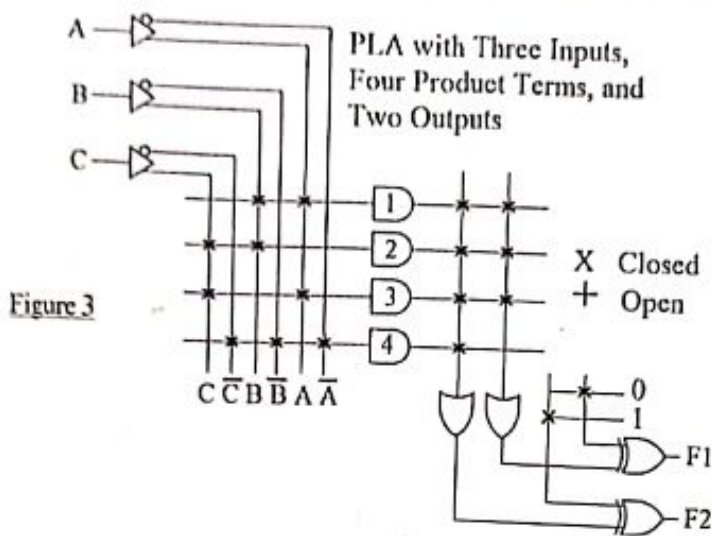- (b) What are the values of  $F_1$  and  $F_2$  in the PLA of Figure 3 in Sum of Products form. Show the ROM Implementation of  $F_1$  and  $F_2$ . What is the size of the ROM used?



$$F_1 = AB + CB + CA$$


$$F_1 = \sum m(3, 5, 6, 7)$$

$$F_2 = (AB) + (CB) + (CA) + (\bar{C}\bar{B}\bar{A})$$

$$F_2 = (\bar{A}\bar{B}C) + (A\bar{B}\bar{C}) + (\bar{A}B\bar{C})$$

$$F_2 = \sum m(1, 2, 4)$$

ROM implementation

 

$\Rightarrow$  A rom of size  $8 \times 2$  is required to implement these 2 Functions.



## 4. [CLO3]


- (a) A sequential circuit with two JK flip-flops A and B and one input X, and one output Z is specified by the following input and output equations:

$$J_A = \overline{B}X, \quad K_A = \overline{B}X, \quad J_B = X, \quad K_B = X, \quad Z = \overline{A}(\overline{B} \oplus X)$$

- Derive the state table.
- Derive the state diagram.
- What is the function of the circuit? Describe in your words.

(4)  
(4)  
(2)

P.S		input	inp A f/F		inp B F/F		No. S		output
A(t)	B(t)	X	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	A(t+1)	B(t+1)	Z
0	0	0	0	0	0	0	0	0	1
0	0	1	1	1	1	1	1	1	0
0	1	0	0	0	0	0	0	1	0
0	1	1	0	0	1	1	0	0	1
1	0	0	0	0	0	0	1	0	0
1	0	1	1	1	1	1	0	1	0
1	1	0	0	0	0	0	1	1	0
1	1	1	0	0	1	1	1	0	0

 


8

The Function is a reverse counter it counts for the sequence 3, 2, 1, 0 and 0 state is reached again it gives output 1 and until the new sequence is started, it gives 1 on output only when next state is 0 again.



 
- (b) Draw the state diagram of a circuit that outputs a 1 when exactly two of the last three serial inputs are 1. e.g., the input sequence of 011011100 produces an output sequence of 001111010. 8/10



No. of states  
can be reduced  
as there are  
redundant states.

5. [CLO3]

 - (a) The Johnson counter advances through the sequence 000, 100, 110, 111, 011, 001 and repeat. Design Johnson counter using D flip-flops. Consider unused states as don't cares. Is your counter self-starting? (Show your work)



P.S			N.S			F/T PLS		
x	y	z	x'	y'	z'	D <sub>A</sub>	D <sub>B</sub>	D <sub>C</sub>
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	0
0	1	0	X	X	X	X	X	X
0	1	1	0	0	1	0	0	1
1	0	0	1	1	0	1	1	0
1	0	1	X	X	X	X	X	X
1	1	0	1	1	1	1	1	1
1	1	1	0	1	1	0	1	1

y z	00	01	11	10
x				
0	1			X
1	1	X		1

$$D_A = \bar{z}$$

y z	00	01	11	10
x				
0				X
1	1	X	1	1


$$D_B = x$$

y z	00	01	11	10
x				
0			1	X
1		X	1	1

$$D_C = y$$

if  $xyz = 010$   
 $x'y'z' = 101$   
 $xyz = 101$   
 $x'y'z' = 010$

 so for unused states  
 010  $\leftrightarrow$  101 if it is  
 not a self-starting  
 counter we have to correct  
 it by taking valid input  
 instead of don't cares.



(b) Design a register cell of an 8-bit register B having following register transfer functions: 9/10

$$C_0: B \leftarrow A \wedge B$$

$$C_1: B \leftarrow A \vee \overline{B}$$

$$C_2: B \leftarrow \overline{B}$$


$$B_i = C_0(A_i B_i) + C_1(A + \overline{B}) + C_2(\overline{B})$$

$$\text{load} = C_0 \overline{C_1} \overline{C_2} + \overline{C_0} \overline{C_1} C_2 + \overline{C_0} C_1 \overline{C_2}$$

~~transfer operation~~ is performed only when when of the three control inputs is one other wise data remain same.

$$(C_0 + C_1 + C_2)$$

 (as there are mutually exclusive operations).





6. [CLO3]

(a) How many address lines and how many data lines a 64M x 8 DRAM chip has?

5/ [5]

$$\text{As } 2^{26} = 64\text{M}$$

so

a 64M x 8 DRAM has 26 address lines and 8 data lines

(b) A 4 GB DRAM uses 4-bit data and has equal-length row and column addresses. How many address pins does the DRAM have?

5/ [5]

32G bits where 4 bit data


$$\text{so } \frac{2^{35}}{2^2} = 2^{33}$$

so it have 33 address lines each address having 4 bits of data.

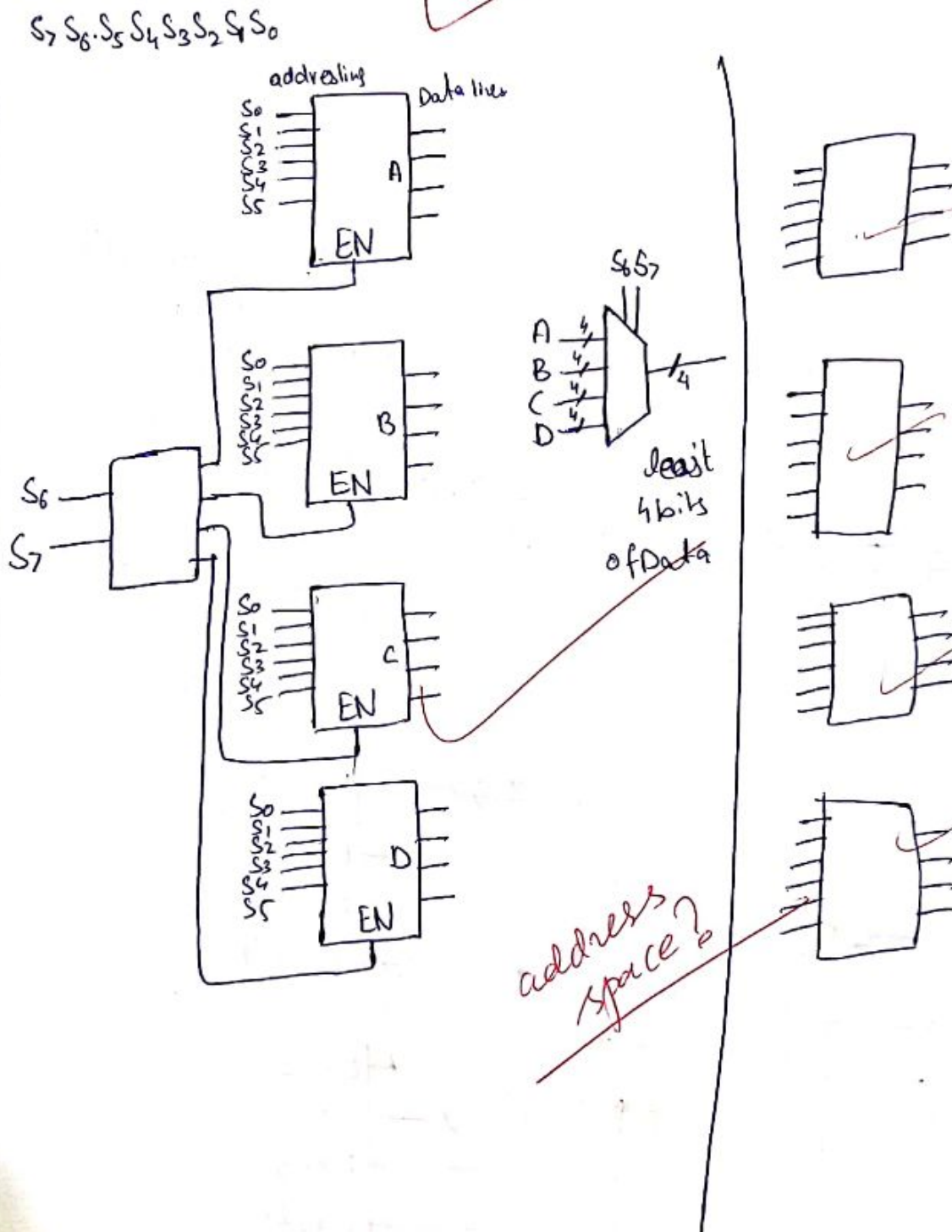- (c) How many  $64 \times 4$  RAM chips (with enable input) are needed to construct a  $256 \times 8$  RAM? Show the external connections. Also mention the address space of each RAM chip. (10)

Hint: Use decoder.

total 8  $64 \times 4$  RAM chips would be used.



## 7. [CLO3]

- (a) The following register transfer operations will be implemented where  $K_1, K_0$  are two input Boolean variables:

$$\overline{K_1} \cdot \overline{K_0}: R1 \leftarrow R2$$

$$\overline{K_1} \cdot K_0: R2 \leftarrow R3$$

$$K_1 \cdot \overline{K_0}: R3 \leftarrow R2$$

$$K_1 \cdot K_0: R1 \leftarrow R4$$

All four n-bit registers  $R1, R2, R3$ , and  $R4$  have three-state bi-directional input/output lines connecting to a single shared bus as shown in the Figure 4 below. Find the values of the the control signals  $Load_i$  and  $EN_i$  of the registers (i.e.,  $Load1, Load2, Load3, Load4, EN1, EN2, EN3$  and  $EN4$ ) so that the above conditional register transfer operations can be realized. Note that  $Load_i$  and  $EN_i$  are functions of  $K_1$  and  $K_0$ .

 


Figure 4

$$Load1 = (\overline{K_0} \cdot \overline{K_1}) + (K_0 \cdot K_1) \\ = (K_0 \oplus K_1)$$

$$Load2 = \overline{K_1} \cdot K_0$$

$$Load3 = K_1 \cdot \overline{K_0}$$


$$Load4 = 0$$

$$EN1 = 0$$

$$EN2 = (\overline{K_1} \cdot \overline{K_0}) + (K_1 \cdot K_0)$$

$$EN3 = (\overline{K_1} \cdot K_0)$$

$$EN4 = (K_1 \cdot K_0)$$

 



- (b) Draw the logic diagram of a 4-bit register (using D flip-flops) with mode selection inputs  $S_1$  and  $S_0$ . The register is to be operated according to the following function table:

$S_1$	$S_0$	Register Operation
0	0	Complement Output
0	1	Clear Register to 0
1	0	No Change
1	1	Load Parallel Data

10 / [10]

